

SUBJECT: DIGITAL ELECTRONICS – I

Day: Wednesday
Date: 24/04/2019

Time: 12.00 NOON TO 02.00 PM
Max Marks: 40

S-2019-1127

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Answers to the right indicate **FULL** marks
- 3) Draw diagrams **WHEREVER** necessary.

Q.1 Answers any **TWO** of the following (10)

- a) Explain the working of 1:4 demultiplexer with necessary diagram.
- b) Simplify the following Boolean expression using K – map and draw its simplified logic diagram.: $Y = \overline{A}BC + \overline{A}\overline{B}C + \overline{A}BC + ABC$
- c) State and prove De – Morgan’s theorems.

Q.2 Answers any **TWO** of the following (10)

- a) Define Encoder. With diagram explain octal to binary encoder.
- b) Give any four basic Boolean postulates and simplify the following expression using Boolean algebra : $A + \overline{A}B = A + B$
- c) With neat diagram explain the working of full adder.

Q.3 Answers any **TWO** of the following (10)

- a) Explain BCD to seven segment decoder with necessary diagram.
- b) Draw the logic symbols and write the truth tables for the following logic gates:
 - i) EX – OR
 - ii) NAND
 - iii) NOR
- c) Convert the following
 - i) $(101101)_2 = (?)_{\text{Gray}}$
 - ii) $(11011)_{\text{Gray}} = (?)_2$

Q.4 Answers any **FIVE** of the following (10)

- a) Define the terms for the logic families:
 - i) Propagation delay time
 - ii) Noise margin
- b) Draw logic diagram of half subtractor.
- c) Define decoder.
- d) Write truth table for 4 : 1 multiplexer
- e) Perform the following
 - i) $(359)_{10} = (?)_8$
- f) What is priority encoder?
- g) Represent the following decimal numbers in 2’s compliment format :
 $(19)_{10}$