

SUBJECT: LINEAR ELECTRONICS – I

Day: Tuesday
Date: 07/05/2019

Time: 12.00 NOON TO 02.00 PM
Max. Marks: 40


S-2019-1126

N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw diagrams **WHEREVER** necessary.
- 4) Use of scientific **CALCULATOR** is allowed.

Q.1 Answer any **TWO** of the following: (10)

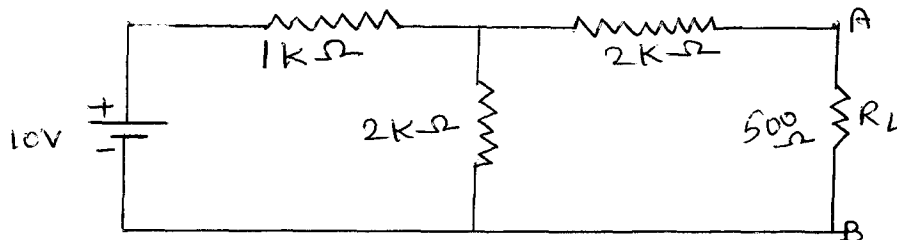- a) With neat diagram explain the output characteristics of transistors in CE- mode.
- b) Draw Thevenin's equivalent for the circuit. Also calculate I_L .



- c) Define capacitance. Explain the action of electrolytic capacitor with necessary diagram.

Q.2 Answer any **TWO** of the following: (10)

- a) Write in detail classification of resistors.
- b) Explain the following terms for JFET:
 - i) Dynamic drain resistance
 - ii) Transconductance
 - iii) Amplification factor and derive the relation between them. Also draw symbol for n- channel JFET.
- c) State the biasing methods for transistor. Explain any one method with necessary diagram.

Q.3 Answer any **TWO** of the following: (10)

- a) Explain the working of UJT with neat diagram.
- b) Draw circuit of single stage RC coupled CE- amplifier.
- c) Explain the working of n-channel MOSFET in depletion mode. Explain the role of coupling and emitter bypass capacitor. Also give the expression for voltage gain of this amplifier.

Q.4 Answer any **FIVE** of the following: (10)

- a) Define α and β for transistor. Derive the expression for α in terms of β .
- b) Define time constant for charging of capacitors.
- c) State Norton's theorem.
- d) Draw the circuit symbols for pnp and npn transistors.
- e) State types of amplifier based on Q- point position.
- f) Draw symbols for step-up and step-down transformer.
- g) State two points of difference between BJT and FET.

* * * *