

**S.Y.B.SC. SEM – IV (CBCS - 2016 Course) : SUMMER - 2019**  
**SUBJECT : PHYSICS : ELECTRONICS**

Day : Saturday  
 Date : 20/04/2019

S-2019-0846

Time : 11.00 A.M. To 02.00 P.M.  
 Max. Marks : 60

**N. B. :**


- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Use of **SCIENTIFIC** calculator is allowed.

**Q.1** Answer **ANY TWO** of the following: (12)

- a) Explain the action of RS- Flip-flop with diagram and truth table.
- b) Explain the Barkhausen criteria for sustained oscillations.
- c) With necessary diagram explain the output characteristics of transistor in CE-mode.

**Q.2** Answer **ANY TWO** of the following: (12)

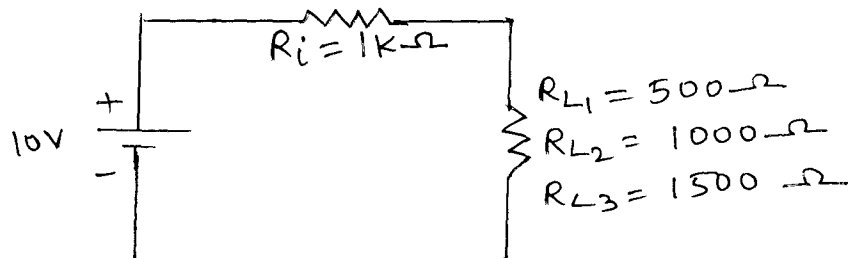- a) i) Give the statement for Maximum power Transfer theorem.
- ii) Verify maximum power transfer theorem for the following circuit.




- b) Convert the following:
  - i)  $(64)_{10} = (?)_8$
  - ii)  $(76)_{10} = (?)_{16}$
  - iii)  $(4BAC)_{16} = (?)_2$
- c) Explain the action of SMPS with duty cycle.

**Q.3** Answer **ANY TWO** of the following: (12)

- a) Draw symbols for UJT and explain its I-V characteristics.
- b) With neat diagram explain the action of full wave rectifier with necessary diagram.
- c) Explain the action of RC coupled amplifier with necessary diagram.

**Q.4** Answer **ANY THREE** of the following: (12)

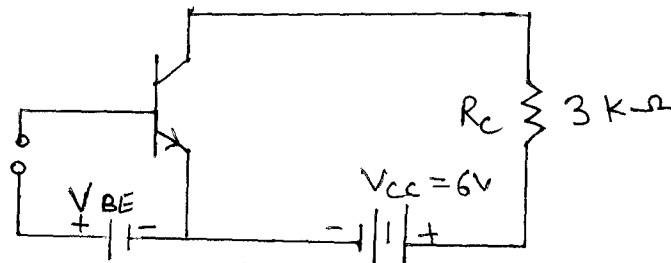- a) In the following circuit diagram if  $V_{cc} = 6V$  and  $R_c = 3k\ \Omega$ , draw d.c. load line. What will be Q- point if zero signal base current is  $20\ \mu A$  and  $\beta = 50$ ?



- b) Give the statement for following:
  - i) Thevenin's theorem
  - ii) Norton's theorem
- c) Explain the following gates with symbol, Boolean expression and truth table
  - i) AND
  - ii) EXOR
- d) Explain the action of transistor as a switch.

**Q.5** Answer **ANY FOUR** of the following: (12)

- a) State any three Boolean laws.
- b) Explain the three pin regulator IC 7905.
- c) State and explain De-Morgans second theorem.
- d) i) Using 1's complement method, subtract  $(01101)_2$  from  $(11011)_2$   
 ii) Using 2's complement method, subtract  $(101)_2$  from  $(111)_2$
- e) Define the following: i) load regulation ii) Line regulation
- f) Find  $\alpha$ ,  $I_B$  and  $I_E$ . Given  $I_C = 10\ mA$  and  $\beta = 200$