

B.Tech. SEM -IV Electronics / Bio Medical 2014 Course (CBCS) :

SUMMER - 2019

SUBJECT: ANALOG INTEGRATED CIRCUITS

(Common for Biomedical & Electronics)

Day: Thursday
Date: 23/05/2019

Time: 10.00 AM TO 01.00 PM
Max. Marks. 60

S-2019-2612

N.B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks
- 3) draw the labeled diagrams **WHEREVER** necessary

- Q.1** a) Draw the op-amp symbol and describe the various op-amp terminals. (07)
b) Write a note on packages of op-amp. (03)

OR

Write a note on frequency response of an op-amp. (10)

- Q.2** a) Draw an op-amp circuit whose output is $V_1 - V_2 + V_3 - V_4$. (07)
b) What are the designing steps of a practical integrator using op-amp. (03)

OR

Derive expression for gain of an instrumentation amplifier employing 3 op-amps. (10)

- Q.3** a) Describe with diagram and waveforms, the principle of operation of an inverting comparator. (06)
b) Draw circuit diagram for temperature compensated antilog amplifier. (04)

OR

Define the following terms related to sample and hold circuit. (10)

- i) Acquisition time ii) Aperture time iii) Droop iv) Feed through v) Hold mode settling time

- Q.4** a) Design a high pass filter at a cut off frequency of 1KHz with a pass band gain of 2. (06)
b) Using frequency scaling technique, convert 1KHz cut off frequency of a high pass filter to a cut off frequency of 1.6KHz. (04)

OR

Draw and describe the working of square and triangular waveform generator using op-amp along with waveforms. (10)

- Q.5** Design an astable multivibrator using IC555 to have output frequency of 2.5 KHz with variable duty cycle from 20% to 80%. Assume $V_{CC}=12V$. (10)

OR

- a) Define following terms related to an IC565 (06)
i) Lock range ii) Capture range iii) Pull-in-time
b) Draw the block diagram of an IC565 PLL. (04)

- Q.6** Discuss the successive approximation analog to digital converter technique with the help of block diagram. (10)

OR

Discuss the working of binary weighted resistor DAC with its circuit diagram. (10)

* * * *