

**B.Tech. SEM -IV Bio Medical 2014 Course (CBCS) : SUMMER - 2019**  
**SUBJECT: DIGITAL LOGIC CIRCUITS**

Day: Thursday  
Date: 30/05/2019

**S-2019-2633**

Time: 10.00 AM TO 01.00 PM  
Max Marks: 60

**N.B.:**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat labeled diagrams **WHENEVER** necessary.

**Q.1** Minimize the following expressions using K-map and realize it using the basic gates. (10)

i)  $Y = \sum m(1, 2, 9, 10, 11, 14, 15)$

ii)  $Y = \sum m(1, 3, 4, 5, 7, 9, 11, 13, 15)$

**OR**

**Q.1** Perform the following using 2's complement method. (10)

i)  $(4)_{10} - (9)_{10}$

ii)  $(-6)_{10} - (-2)_{10}$

iii)  $(9)_{10} - (4)_{10}$

iv)  $(6)_{10} - (6)_{10}$

v)  $(11010)_2 - (10000)_2$

**Q.2 a)** What is meant by a priority encoder? Give example. (06)

**b)** What is a Multiplexer? State applications of Multiplexers. (04)

**OR**

**Q.2 a)** Describe Excess-3 adder with the help of neat diagram. (06)

**b)** Design 5 bit magnitude comparator using comparator IC7485. (04)

**Q.3 a)** What do you mean by tristate logic? Describe in detail one application of such logic circuit. (06)

**b)** Describe the operation of Tristate buffer. (04)

**OR**

**Q.3** Describe the following Logic families: (10)

i) TTL      ii) CMOS      iii) ECL

**Q.4** Carry out the following Flip Flop conversions: (10)

i) J-K to D    ii) J-K to T    iii) S-R to T

**OR**

**Q.4** Describe Mealy and Moore model with a help of an example. (10)

**Q.5** Implement MOD-12 ripple counter using J-K Flip Flop and describe its working. (10)

**OR**

**Q.5 a)** State various applications of shift registers. (06)

**b)** Draw logic diagram and waveform of twisted ring counter. (04)

**Q.6** A combinational circuit is defined by the function (10)

$F_1(A, B, C) = \sum m(4, 5, 7)$

$F_2(A, B, C) = \sum m(3, 5, 7)$  Implement the circuit with a PLA having three input three product terms and two outputs.

**OR**

**Q.6** Classify the semiconductor memories in detail. (10)

\*      \*      \*      \*