

**B. Tech. Sem -III (E & TC Engg.) (2014 COURSE) (CBCS) :
SUMMER - 2019**

SUBJECT: DIGITAL CIRCUITS & APPLICATIONS

Day: Tuesday
Date: 14/05/2019

S-2019-2589

Time: 02.30 PM TO 05.30 PM
Max Marks. 60

N.B.:

- 1) All questions are **COMPULSORY**.
 - 2) Figures to the right indicate **FULL** marks
 - 3) Draw the labeled diagrams **WHEREVER** necessary
-

- Q.1**
- a) What is binary no? Discuss the procedure to convert **(05)**
i) Binary number to decimal number.
ii) Decimal number to binary number.
- b) Simplify following expression using k-map and draw logic diagram **(05)**
 $F = \pi M (0, 1, 3, 5, 6, 7, 10, 14, 15)$

OR

- a) What are the basic rules of Boolean algebra? **(05)**
- b) Design a combinational logic circuit having 3 input, & output is equal to 1, if input variable have more 1's than 0's otherwise the output is 0. **(05)**
- Q.2**
- a) Implement the following Boolean function using 8:1 MUX **(05)**
 $f(A,B,C,D) = \sum m (0,1,3,4,8,9,15)$
- b) What is full adder? Design a full adder using two half adders. **(05)**

OR

- a) How do you convert binary no. to corresponding gray code using a code converter? **(05)**
- b) What do you mean by De-MUX? Explain it with one example. **(05)**
- Q.3**
- a) Draw CMOS inverter diagram. **(03)**
- b) Define following **(07)**
i) Fan in ii) Fan out iii) Noise margin
iv) Power dissipation v) Propagation delay.

OR

- a) What are logic families? Explain any one in detail. **(05)**
- b) What is meant by TTL? Explain any one configuration of TTL family **(05)**
- Q.4**
- a) Design and explain RS-latch using NOR gates. **(05)**
- b) What is the classification of sequential machine? Explain in detail. **(05)**

P.T.O.

OR

- a) What is D-flip flop? Draw and explain it with truth table. (05)
- b) What is the purpose behind state reduction? Find out reduced state diagram for following state table using state reduction. (05)

Present state	Next state		Output	
	X=0	X=1	X=0	X=1
a	a	b	0	0
b	c	d	0	0
c	d	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

- Q.5** a) What are the applications of shift registers? Explain any one in detail. (05)
- b) Design and explain 4 bit asynchronous up counter. (05)

OR

- a) What is modules counter? Explain MOD-4 counter in detail. (05)
- b) What is meant by Bidirectional shift register? Explain it with neat diagram. (05)

- Q.6** a) A combinational circuit is defined by function (05)
 $F_1 = \sum m(1,5,7)$
 $F_2 = \sum m(5,6,7)$
Implement the circuit with PLA

- b) What is classification of RAM? Explain any one in detail. (05)

OR

- a) Explain basic memory operation with suitable block diagram. (05)
- b) What is the difference between PAL & PLA and PROM? (05)

* * * *