

B.Tech SEM-IV Biomedical (2014 Course) CBCS: SUMMER-2019
SUBJECT: ELECTRONIC CIRCUITS AND APPLICATIONS

Day: Saturday
 Date: 25-05-2019

Time: 10:00 AM TO 1:00 PM
 Max Marks: 60

S-2019-2613-A


N.B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat diagrams **WHEREVER** necessary.
- 4) Use of scientific calculator is **ALLOWED**.

- Q.1** Write short note on : **(10)**
- i) Effect of cascading on overall gain and bandwidth in multistage amplifiers.
 - ii) Choice of transistor configuration in cascade amplifier.

OR

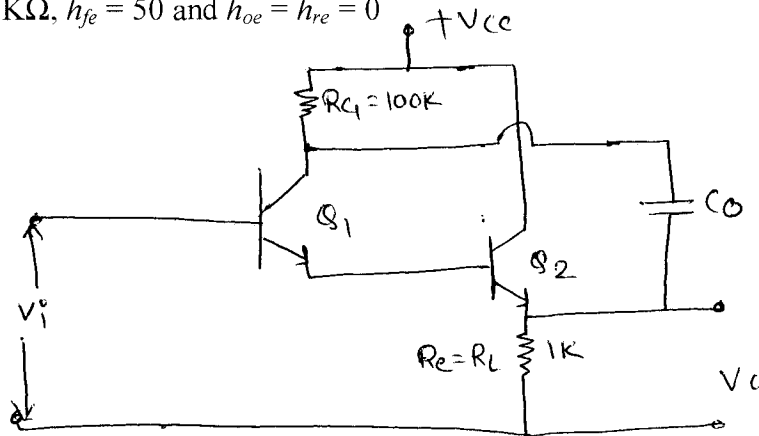
- Q.1** For the circuit shown in the figure calculate R_i , A_i , A_v for each stage and also calculate overall voltage gain. Both transistors are identical having $h_{ie}=1.1K\Omega$, $h_{fe}=50$ and $h_{oe}=h_{re}=0$ **(10)**



- Q.2** Discuss the advantages and disadvantages of negative feedback. **(10)**

OR

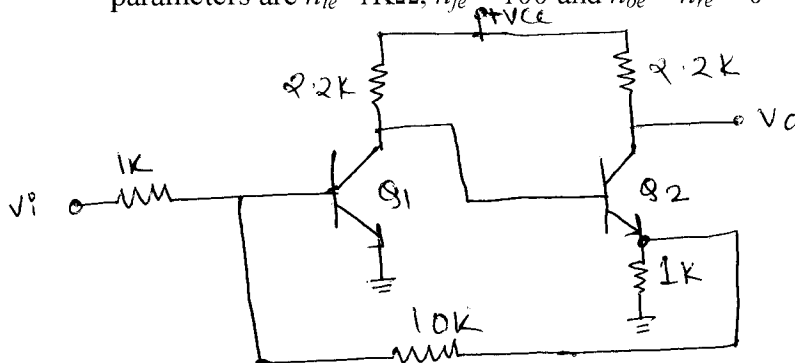- Q.2** For the Circuit shown in the figure calculate A_{vf} , R_{if} , and R_{of} . Transistor parameters are $h_{ie}=1K\Omega$, $h_{fe}=100$ and $h_{oe}=h_{re}=0$ **(10)**



- Q.3** What are the different distortions those occur in an AF power amplifier? Describe how even harmonics get eliminated in Class A push pull amplifier. **(10)**

OR

- Q.3** a) What is thermal resistance? Describe the thermal electrical analogy related to a transistor with heat sink. **(05)**
 b) What is heat sink? What is its function? **(05)**

P.T.O.

Q.4 Describe the working of Wien bridge oscillator with the help of circuit diagram. Derive the expression for its frequency of oscillation. **(10)**

OR

Q.4 A quartz crystal has the following constants, $L = 50\text{mH}$, $C_1 = 0.02\text{pF}$, $R = 500\Omega$ and $C_2 = 12\text{pF}$. Find the values of f_s and f_p . If the external capacitance across the crystal changes from 5pF to 6pF , find the change in frequency of oscillations. **(10)**

Q.5 What are the different performance factors of a regulator? Define. **(10)**

OR

Q.5 Draw and design a series transistor voltage regulator circuit to provide output of 15V for a maximum load current of 2A , when the input voltage variation is 20 to 23V and transistor gain is 50 . **(10)**

Q.6 Draw hybrid- π equivalent circuit of a high frequency BJT. Describe the significance of each component in the equivalent circuit. **(10)**

OR

Q.6 A common emitter single stage HF amplifier uses a resistive load R_L . Using the hybrid π equivalent circuit derive an expression for current gain at high frequency. **(10)**

* * *