

**B. Tech. Sem -III (E & TC Engg.) (2014 COURSE) (CBCS) :  
SUMMER - 2019**

**SUBJECT : NETWORK THEORY**

Day : Wednesday  
Date : 15/05/2019


Time : 02.30 PM TO 05.30 PM  
Max. Marks : 60

S-2019-2590


**N. B. :**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labeled diagram **WHEREVER** necessary.
- 4) Use of non-programmable calculator is **ALLOWED**.
- 5) Assume suitable data, if necessary.

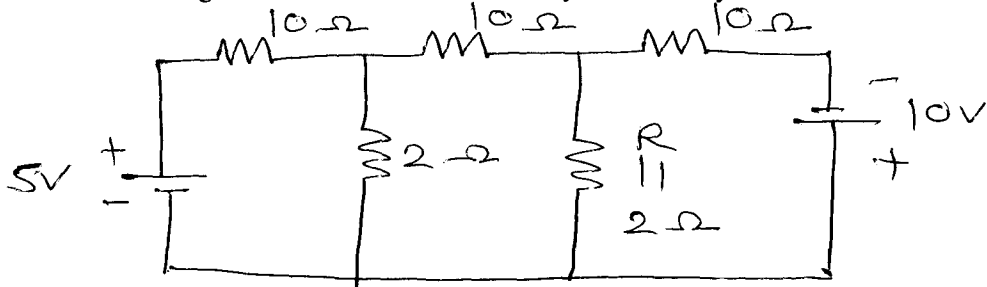
**Q.1 a) Find the voltage across R in the network by mesh analysis: (05)**



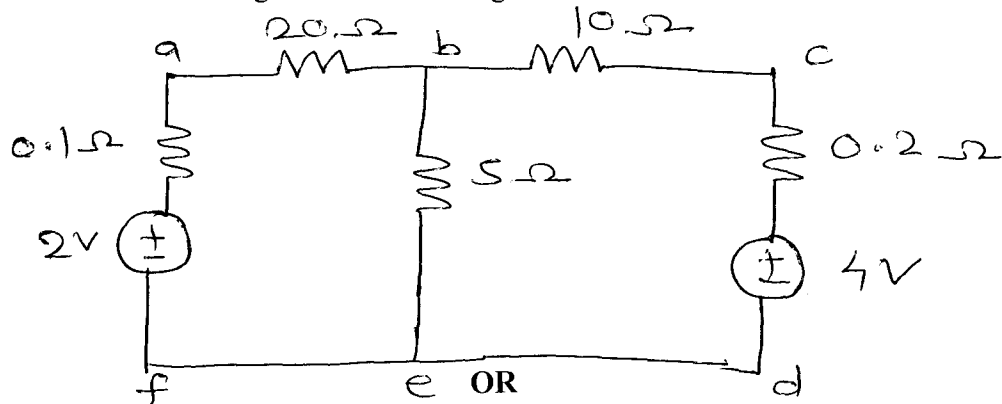
**b) Find current through branch b-e using Norton theorem: (05)**



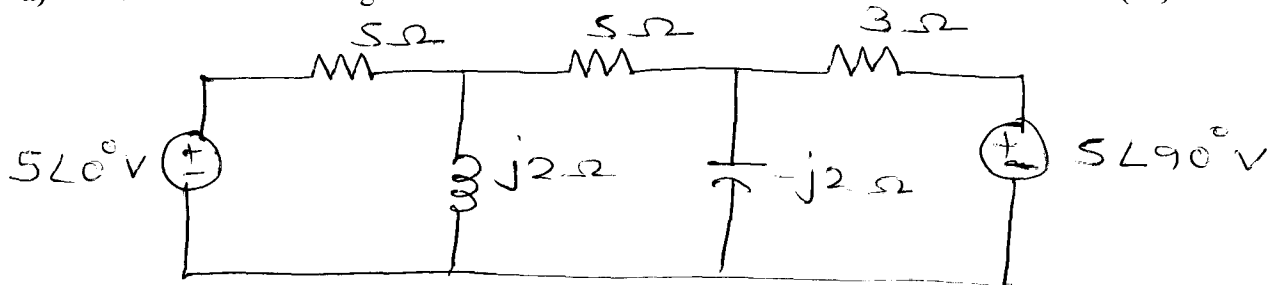**a) Determine node voltages for the shown network: (05)**



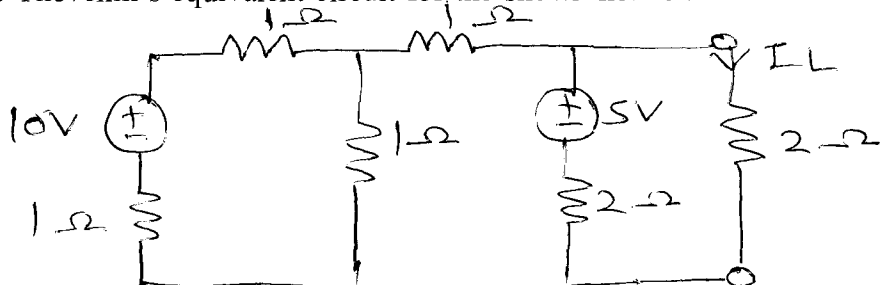**b) Draw the Thevenin's equivalent circuit for the shown network and find load current: (05)**




**P. T. O.**

- Q. 2 a) What is tree and what are the properties of tree? (05)  
 b) Draw the oriented graph from reduced incidence matrix: (05)


$$A = \begin{bmatrix} 0 & 0 & -1 & 1 & -1 & 0 \\ -1 & 1 & 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 1 & -1 \end{bmatrix}$$

OR

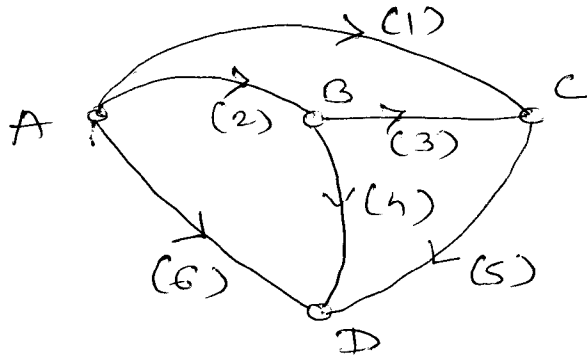- a) What is the use of network equilibrium equation? (05)  
 b) Find the proper cut-sets for the following graph: (05)



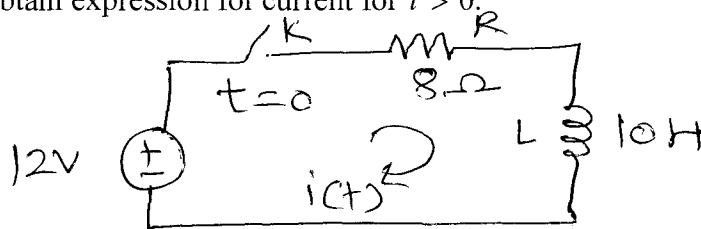- Q. 3 a) In the circuit shown switch is kept open for long time. At  $t = 0$  it is closed. (05)  
 Obtain expression for current for  $t > 0$ .



- b) For series RL circuit (05)  
 Find:  $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$  at  $t = 0^+$  Where  $V = 200V, R = 5 \Omega$  and  $L = 3H$

OR

- a) Find transient response of driven R-C circuit (05)  
 b) What are the initial conditions of passive components? (05)


- Q. 4 a) Find effect of anti-resonance on selectivity and bandwidth. (04)  
 b) A practical parallel resonant circuit consists a coil of 0.1 H inductance with  $10 \Omega$  leakage resistance with a  $10 \mu F$  capacitor in parallel with it. Find frequency at which current in the circuit which is properly resistive. Also find impedance under resonance. (06)

OR

- a) A series resonant circuit has impedance of  $500 \Omega$  at resonant frequency, cut-off frequencies are 10 KHz and 100 KHz. Determine: (07)  
 i) Resonant frequency  
 ii) Value of R, L, C components  
 iii) Quality factor at resonant frequency

b) What is anti-resonance and what is the application of the same? (03)

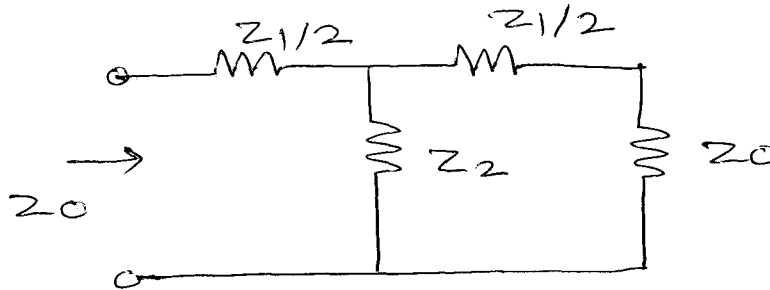Q. 5 a) Derive  $Z_o$  for given network: (05)




b) A  $\pi$  - Low pass filter network consists of a series arm inductance of 20 mH and two shunt arm capacitor of 0.16  $\mu$ F each. Calculate cut-off frequency, attenuation and phase shift at 1.5 KHz. (05)

OR

a) What are the design formulae of K-high pass filter? (05)

b) Design k-T section LPF to be terminated into  $1k\Omega$  and having a cut-off frequency of 3 KHz. Determine frequency at which filter offers an attenuation of 20dB. (05)

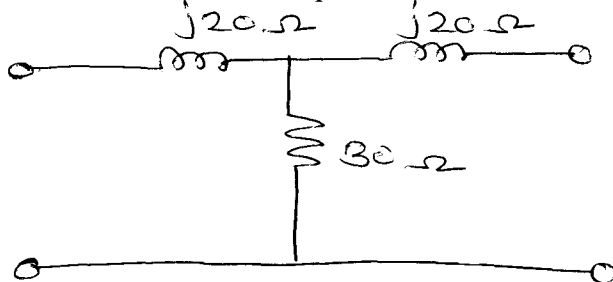Q. 6 a) For the network shown determine Z and Y parameter. (05)



b) Derive Z parameter in terms of ABCD parameter. (05)

OR

a) Find symmetry and reciprocity conditions of h parameters. (05)

b) When two networks are connected in parallel find y parameters for the combined network. (05)