

**S.Y.B.SC. (COMPUTER SCIENCE) SEM –IV (2014 COURSE) :**  
**SUMMER - 2018**  
**SUBJECT : COMPUTER INSTRUMENTATION**

Day : **Tuesday**  
Date : **24/04/2018**

**S-2018-0854**

Time : **03.00 PM TO 05.00 PM**  
Max. Marks : 40

---

**N.B.:**

- 1) All questions are **COMPULSORY**.
  - 2) Figures to the right indicate **FULL** marks.
  - 3) Draw diagrams **WHEREVER** necessary.
- 

**Q.1** Answer **ANY TWO** of the following: **[10]**

- a) Explain voltage to frequency convertor with necessary diagrams.
- b) Explain the following parameters for sensors:  
i) Accuracy ii) Linearity iii) Sensitivity iv) Resolution v) Range.
- c) Draw circuit diagram of Wheatstone's bridge. Explain the balanced condition for its working.

**Q.2** Answer **ANY TWO** of the following: **[10]**

- a) Explain the working of Linear Variable Differential Transformer with necessary diagram.
- b) What are filter circuits? Explain with diagram basic principle of RC filter circuit.
- c) With neat diagram explain the block diagram of water level indicator system using float switch.

**Q.3** Answer **ANY TWO** of the following: **[10]**

- a) Explain signal conditioning system with necessary diagram.
- b) Draw diagram of three OP-AMP instrumentation amplifier and explain it.
- c) Write short note on tilt sensor.

**Q.4** Answer **ANY FIVE** of the following: **[10]**

- a) What is band pass filter?
- b) State the types of temperature sensors.
- c) How is analysis of ECG signal done?
- d) State two points of difference between active and passive filters.
- e) Give any two applications of Quantum dots.
- f) State the features of AD 590.
- g) State any two applications of infrared radiation.

\* \* \* \*

---