

F.Y.B.SC. (COMPUTER SCIENCE) SEM –II (2014 COURSE) :
SUMMER - 2018

SUBJECT : DIGITAL ELECTRONICS – II

Day : **Wednesday**
Date : **25/04/2018**

S-2018-0841

Time : **03.00 PM TO 05.00 PM**
Max. Marks : 40

N.B.:

- 1) All questions are **COMPULSORY**.
 - 2) Figures to the right indicate **FULL** marks.
 - 3) Draw neat and labeled diagrams **WHEREVER** necessary.
-

Q.1 Answer **ANY TWO** of the following: [10]

- a) Construct the following counters using IC 7490:
i) MOD 2 ii) MOD 10
- b) Explain the action of 3-bit shift register in serial-in-serial-out mode.
- c) Explain the monostable mode of IC 555. Draw the necessary waveforms.

Q.2 Answer **ANY TWO** of the following: [10]

- a) Describe working of J-K flip-flop with logic diagram and truth table.
- b) Explain four bit synchronous counter in detail.
- c) Write short notes on : PROM and EPROM.

Q.3 Answer **ANY TWO** of the following: [10]

- a) Explain R-S flip-flop using NAND gates with symbol, logic diagram and truth table.
- b) A timer 555 is configured to turn in astable mode with $R_A = 4k\Omega$, $R_B = 4k\Omega$ and $C = 0.01\mu F$. Determine the frequency of the output and duty cycle.
- c) What is a ring counter? Explain with diagram and truth table 4-bit ring counter.

Q.4 Answer **ANY FIVE** of the following: [10]

- a) State the truth table for T-flip-flop and D-flip-flop.
- b) What is a bistable multivibrator? Give any one application.
- c) What is race around condition in J-K flip-flop? How is it avoided?
- d) Define modulus of a counter. Find the number of flip-flops required for MOD5 counter.
- e) Draw input and output waveforms of bistable multivibrator.
- f) State the difference between synchronous and asynchronous counters.
- g) Define Preset and Clear terminals in flip-flop.

* * * *