

B. TECH. SEM - III (ELECTRONICS) 2014 COURSE) (CBCS) :
SUMMER - 2018
SUBJECT: DIGITAL LOGIC CIRCUITS

Day: **Thursday**
Date: **24/05/2018**

S-2018-2247

Time: **02.30 PM TO 05.30 PM**
Max Marks. 60

N.B.

- 1) All questions are **COMPULSORY**.
 - 2) Figures to the right indicate **FULL** marks.
 - 3) Assume suitable data , if necessary.
 - 4) Draw neat diagram **WHEREVER** necessary.
-

Q.1 Minimize the following expressions using K – map and realize the same using basic gates. (10)

i) $Y = \sum m(1,3,4,5,7,9,11,13,15)$

ii) $Y = \sum m(1,2,9,10,11,14,15)$

OR

Q.1 Discuss the following reduction techniques with the help of advantages and disadvantages. (10)

- i) Simplification using Boolean algebra laws
- ii) Karnaugh map
- iii) Quine Mccluskey method

Q.2 a) Design a parity generator using the basic gates to produce digital words with odd parity. Assume the input to be three bit binary words. (06)

b) Compare Encoder and decoder (04)

OR

Q.2 Design and implement a 2-bit comparator using suitable gates. (10)

Q.3 Describe the following three types of output configurations. (10)

- i) Open Collector output
- ii) Totem pole output
- iii) Three state or tristate output

OR

Q.3 Describe the following term with respect to logic families & give their typical values for standard TTL, CMOS & ECL families. (10)

- i) Fan-out
- ii) Propagation Delay
- iii) Noise margin
- iv) figure of merit

Q.4 Write the state table, draw the state diagram and write the state equation for the following flip flops. (10)

- i) Clocked D flip flop
- ii) Clocked JK FF

P.T.O

OR

Q.4 a) Describe the working of master slave JK flip-flop with the help of neat diagram. (06)

b) What is the function of preset and clear inputs in flip-flop? (04)

Q.5 a) Design a Modulo-5 ripple counter using a 3 bit ripple counter. (06)

b) Compare synchronous & Asynchronous counter. (04)

OR

Q.5 Design a sequence generator using JK flip flops
1001001 (10)

Q.6 Compare the following : (10)

i) RAM & ROM

ii) SRAM & DRAM

iii) EPROM & EEPROM

OR

Q.6 Design and implement 3 – bit Binary to Gray code converter using PLA. (10)

*

*

*