

B.TECH. SEM -IV ELECTRONICS / BIO MEDICAL 2014

COURSE (CBCS) : SUMMER - 2018

SUBJECT: ELECTRONIC CIRCUITS AND APPLICATIONS

Day: Tuesday
Date: 05/06/2018

S-2018-2292

Time: 10.00 AM TO 01.00 PM
Max. Marks: 60


N.B:

- 1) All questions are **COMUPLSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Use of non-programmable **CALCULATOR** is allowed.
- 4) Draw neat and labeled diagram **WHEREVER** necessary.

Q.1 Discuss the various schemes to couple the output of first stage to the input of second stage in two amplifiers with the help of circuit diagrams. **(10)**

OR

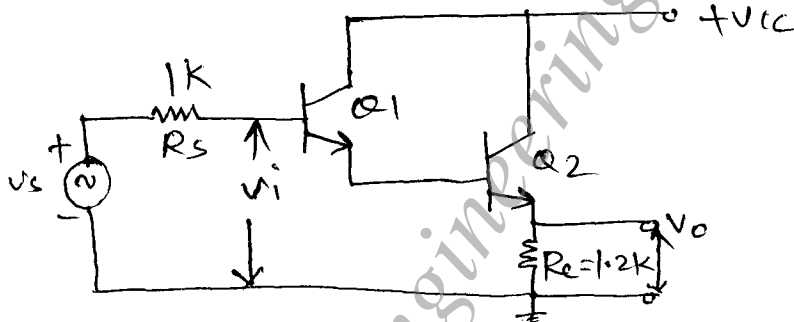Q.1 For Darlington pair emitter follower shown in the following figure Q_1 has $h_{ie1} = 8K\Omega$, $h_{fe1} = 80$, $h_{re1} = h_{oe1} = 0$ and Q_2 has $h_{ie2} = 1.5 K\Omega$, $h_{fe2} = 100$, $h_{re2} = h_{oe2} = 0$, determine i) R_i ii) A_v iii) A_f iv) R_o **(10)**



Q.2 a) If an amplifier with lower 3dB frequency f_L , upper 3dB frequency f_H and mid-frequency gain A_{mid} is used in feedback application with feedback factor β , show that: lower 3dB frequency of the feedback amplifier $(f_{L,f}) = \frac{f_L}{1 + \beta A_{mid}}$ and upper 3 dB frequency of the feedback amplifier $(f_{Hf}) = f_H (1 + \beta A_{mid})$. **(06)**

b) Describe transconductance and transresistance amplifier. **(04)**

OR

Q.2 Determine the voltage gain, input and output impedance with feedback for voltage series feedback having $A = -100$, $R_i = 10K\Omega$, $R_o = 20K\Omega$ for feedback of i) $\beta = -0.1$ and ii) $\beta = -0.5$ **(10)**

Q.3 Derive the expressions for efficiency of class A power amplifier with: **(10)**
i) Resistive load (series fed)
ii) Transformer coupled load

OR

Q.3 a) Describe the working of complementary symmetry class B amplifier. **(06)**

b) Explain origin of crossover distortion. Describe a method to minimize this distortion. **(04)**

P.T.O.

- Q.4** Draw equivalent circuit of a quartz crystal. Describe significance of each component of the equivalent circuit. Draw circuit diagram of Pierce crystal oscillator and explain its working. **(10)**

OR

- Q.4 a)** Calculate the component values of the Wien bridge suitable to be used in the oscillator to vary the frequency from 200Hz to 20KHz in the two ranges. **(06)**

- b)** In Colpitts oscillator, the frequency of oscillations is observed to be 2.5 MHz oscillator uses: $L = 20 \mu H, C_1 = 0.04 \mu F$ **(04)**

Find: i) Value of C_2 ii) If L is doubled, the new value of frequency of oscillations.

- Q.5 a)** Describe the internal structure of IC 723 with the help of simplified functional block diagram. **(06)**

- b)** List the important features of the regulator IC 723. **(04)**

OR

- Q.5** An emitter follower voltage regulator is to supply a load current 0-2A at 10V. The unregulated DC supply varies from 14V to 18V. Use a zener diode with $V_z = 8.5V$ and which requires a minimum of 1mA current for stable operation. The series transistor has $h_{fe} = 50$ and $V_{BE} = 0.5V$. Determine, **(10)**

i) Value of resistor R to be connected between collector and base of transistor and its wattage rating.

ii) Maximum power dissipation rating for zener diode and transistor.

- Q.6 a)** Derive the equation for g_m , which gives relation between g_m , I_C and temperature. **(05)**

- b)** Define f_β and f_T . What is the relationship between f_β and f_T . **(05)**

OR

- Q.6** For a BJT amplifier the following values are known: **(10)**

Operating temperature $T = 300^{\circ}K, I_{CQ} = 2.5 \text{ mA}$

$r_{bb'} = 100 \Omega, r_{b'e} = 1K \Omega, r_{b'c} = 2M \Omega, r_{ce} = 80K \Omega, C_{b'e} = 200 \text{ pF}$

$C_{b'c} = 3 \text{ pf}, f_T = 70 \text{ MHz}$. Obtain the h- parameters if $K = 1.381 \times 10^{-23} \text{ J}^{\circ}k$ and

$q = 1.6 \times 10^{-19} \text{ C}$.

* * * *