

B. TECH. SEM -III (E & TC ENGG.) (2014 COURSE) (CBCS) :
SUMMER - 2018
Subject: Electronic Devices & Applications

Day: **Tuesday**
 Date: **22/05/2018**

S-2018-2267

Time: **02.30 PM TO 05.30 PM**
 Max. Marks : 60

N.B.:


- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Assume suitable data if necessary.

Q.1 Explain in detail compensation techniques; Thermistor and diode compensation. (10)

OR

Q.1 Draw a voltage divider bias circuit and derive an expression for stability factor. (10)

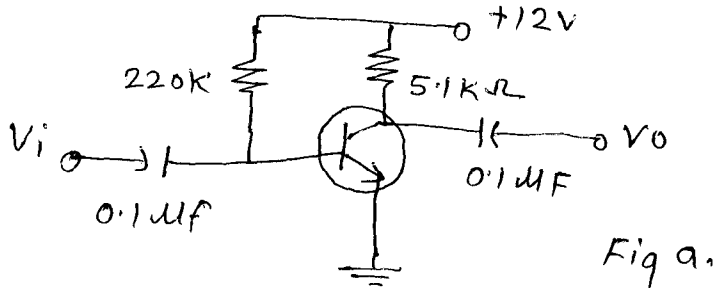Q.2 Determine the input impedance, output impedance, Voltage gain and current gain for the CE amplifier of figure. The h-parameters of the transistor of $h_{fe} = 60$, $h_{ie} = 500 \Omega$ at $I_c = 3mA$. (10)



OR


Q.2 Derive the equations for voltage gain, current gain, input impedance and output admittance for a BJT using low frequency h-parameter model for
 a) CE configuration b) CB configuration c) CC configuration (10)

Q.3 Explain following FET biasing in detail (10)
 i) Self bias ii) Fixed bias iii) current source bias

OR

Q.3 Explain construction, VI characteristic, transfer characteristic of JFET in detail. (10)

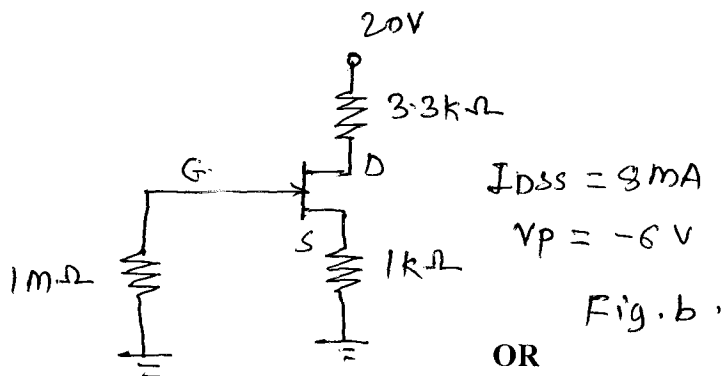Q.4 Determine V_{gs} , I_D , V_{DS} and V_G for the circuit show in fig. b. (10)



OR

Q.4 With the help of suitable diagram explain different types of MOSFET. (10)

Q.5 Explain basic clamper circuit. Classify and explain their different types with its application in detail. **(10)**

OR

Q.5 Explain with suitable diagram Astable multivibrator and monostable multivibrator circuit using BJT. **(10)**

Q.6 Write a construction, VI characteristics and applications of photoconductive cell and photovoltaic cell. **(10)**

OR

Q.6 Write a short note on: **(10)**
i) PCB design Rule
ii) Layout design
iii) Artwork design

* * * *