

B.TECH SEM - III (2007 COURSE) (ELECTRICAL ENGG.) :

SUMMER - 2018

SUBJECT : ELECTRONICS DEVICES AND CIRCUITS

Day: **Wednesday**
Date: **23/05/2018**

S-2018-2573

Time: **02.30 PM TO 05.30 PM**
Max Marks: 80

N. B. :

- 1) **Q. No. 1 and Q. No. 5 are COMPULSORY.** Out of the remaining attempt **ANY TWO** questions from each section.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Answers to both the sections should be written in **SEPARATE** answer book.
- 4) Use of non programmable **calculator** is allowed.
- 5) Assume suitable data if **necessary**.
- 6) Draw neat diagrams wherever necessary.

SECTION - I

- Q.1** a) What is biasing of transistor? Draw circuit diagram of voltage divider bias and write down equation for selection of operating point. (06)
b) Write down equation for current gain in CE and CB configuration. State relationship between them. (04)
c) Draw symbol of opto-coupler and state applications of it. (04)
- Q.2** a) Draw circuit diagram of two stage RC coupled amplifier. State the effect of cascading on gain and band width of amplifier. (07)
b) Draw circuit diagram to plot characteristics of NPN transistor in common base configuration. Show range of instruments used. Draw output characteristics and show all regions on it. (06)
- Q.3** a) Compare class A, class B, class C power amplifiers. (05)
b) Draw schematic diagram of different types of feedback in amplifiers and write the equation for gain with feedback in all types of amplifiers. (08)
- Q.4** a) Draw diagram and describe construction, principle of operation and characteristics of DIAC. State its applications. (07)
b) Compare LED and LCD and state specifications and applications of it. (06)

SECTION - II

- Q.5** a) Why are NAND and NOR gates called as universal gates? Explain. (04)
b) What is the difference between asynchronous and synchronous counter? Explain with block diagram. (05)
c) Write a note on fixed positive voltage regulator IC 78XX series. (05)
- Q.6** a) Explain working of 4 bit adder with neat block diagram. (07)
b) Convert SR flip-flop to JK flip-flop. (06)
- Q.7** a) Explain the operation of RAM, NVRAM, SRAM and DRAM. (07)
b) Design MOD-10 counter using IC 7490 (06)
- Q.8** Draw a Dual tracking Regulated power supply with specifications to deliver 5V to 10V voltage and 1A current. (13)

* * * * *