

B.TECH SEM – IV(2007 COURSE) (ELECTRONICS) : SUMMER

- 2018

SUBJECT: LINEAR INTEGRATED CIRCUITS

Day : **Saturday**
Date : **09/06/2018**

S-2018-2623

Time : **10.00 AM TO 01.00 PM**
Max. Marks: 80

N. B. :

- 1) **Q. No.1 and Q. No. 5 are COMPULSORY.** Out of remaining attempt **Any TWO** questions from each section.
- 2) Figures to the right indicate **FULL** marks.
- 3) Answers to both the sections should be written in the **SEPARATE** answer book.
- 4) Neat diagrams must be drawn **WHEREVER** necessary.

SECTION-I

- Q.1**
- a) Draw the OPAMP symbol and explain the various op-amp terminals. (05)
 - b) Write the difference between OPAMP and Norton amplifier (05)
 - c) Draw the circuit diagram for temperature compensated antilog amplifier. (04)
- Q.2**
- a) Discuss the working of Wilson current source with a neat circuit diagram. (07)
 - b) Define following characteristics of an OPAMP. Also state their ideal values. (06)
i) CMRR ii) Slew rate iii) Bandwidth
- Q.3**
- a) Draw the circuit diagram for basic differentiator. Derive its output equation and draw its output waveforms for sine and square wave input. (07)
 - b) Write a short note on graphic equalizer. (06)
- Q.4**
- a) Draw the circuit diagram of inverting schmitt trigger circuit and derive equations for V_{UT} and V_{LT} . (07)
 - b) Draw the circuit diagram and waveforms of full wave precision rectifier and derive its output for sine wave input. (06)

SECTION-II

- Q.5**
- a) Using multiplier IC, describe voltage squarer with neat circuit diagram. (04)
 - b) Discuss FM demodulation using PLL. (06)
 - c) State and explain any one application of V to I converter. (04)
- Q.6**
- a) With neat circuit diagram, discuss triangular wave generator using op-amp. Write formula for frequency of oscillation. (07)
 - b) Draw and discuss functional block diagram of IC 566. (06)
- Q.7**
- a) Discuss frequency multiplier using PLL with circuit diagram. (07)
 - b) State and describe any one application of power amplifier IC LM380. (06)
- Q.8**
- a) With neat circuit diagram describe V to I converter for grounded load. (07)
 - b) Discuss F to V converter using IC LM331. (06)

* * * * *