

B.TECH SEM – V (2007 COURSE) (BIOMEDICAL ENGG.) :
SUMMER - 2018
SUBJECT: LINEAR INTEGRATED CIRCUITS

Day : **Thursday** Time : **10.00 AM TO 01.00 PM**
Date : **24/05/2018** S-2018-2692 Max. Marks: 80

N.B.:

- 1) Q. No. 1 and Q. No.5 are **COMPULSORY**. Out of remaining attempt **ANY TWO** questions from Section – I and Section – II.
 - 2) Figures to the right indicate **FULL** marks.
 - 3) Answers to both the sections should be written in **SEPARATE** answer books.
 - 4) Draw neat and labeled diagram **WHEREVER** necessary.
 - 5) Assume suitable data, if necessary.
-

SECTION - I

- Q. 1**
- a) Write a short note on single supply operation of an op-amp. (05)
 - b) Compare Schmitt trigger and comparator. (05)
 - c) Draw the circuit diagram of an instrumentation amplifier using 3 op-amp. (04)
- Q. 2**
- a) What is meant by input offset voltage? How it can be compensated? (07)
 - b) Discuss the working of Wilson current source with a neat circuit diagram. (06)
- Q. 3**
- a) Discuss the working of sample and hold circuit. State its applications. (07)
 - b) Define the following terms related to comparator: (06)
 - i) Accuracy
 - ii) Response time
 - iii) Logic threshold
- Q. 4**
- a) What are the disadvantages of an ideal differentiator? Draw a neat circuit diagram of practical differentiator and state equation for f_a and f_b . (07)
 - b) Write a short note on Peaking amplifier. (06)

SECTION - II

- Q. 5**
- a) What are the advantages of active filters over passive filters? (06)
 - b) Draw pin diagram of function generator IC 8038. (04)
 - c) Discuss squarer circuit using multiplier IC. (04)
- Q. 6**
- a) Design a 1st order low pass butter worth filter at a cutoff frequency of 1kHz with a pass band gain of 2. (07)
 - b) Draw and explain circuit diagram of active notch filter. What is Twin-T notch filter? (06)
- Q. 7**
- a) Design a triangular waveform generator for an output frequency of 1.1 kHz and peak to peak amplitude of triangular waveform is 4.94 V_{P-P} and op-amp saturation voltage is 14 v. (07)
 - b) Draw and explain with waveforms, the operation of missing pulse detector using IC 555. (06)
- Q. 8**
- a) Describe with neat circuit diagram, operation of dual slope analog to digital converter. (07)
 - b) Describe any two applications of an IC LM 380. (06)

* * * * *