

B.TECH. SEM -IV ELECTRICAL 2014 COURSE (CBCS) :
SUMMER - 2018
SUBJECT : NETWORK ANALYSIS

Day : **Thursday**
 Date : **07/06/2018**


Time : **10.00 AM TO 01.00 PM**
 Max. Marks : 60

S-2018-2288

N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Use of non-programmable **CALCULATOR** is allowed.
- 4) Assume suitable data if necessary.

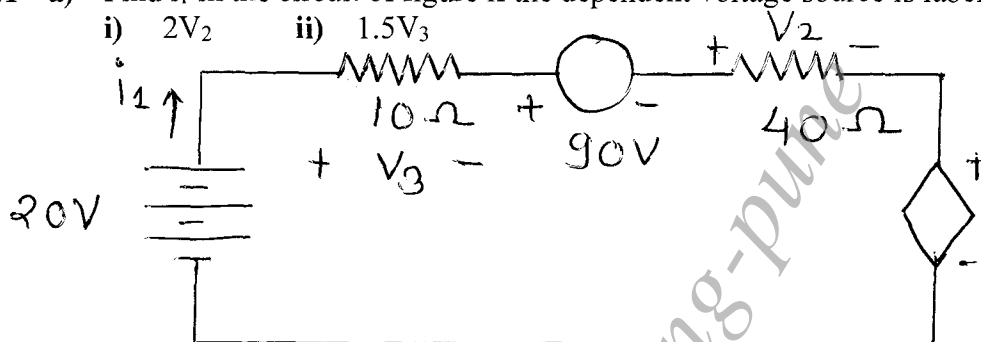
Q.1 a) Find i_1 in the circuit of figure if the dependent voltage source is labeled: **[05]**




b) State and explain Reciprocity theorem. **[05]**

OR

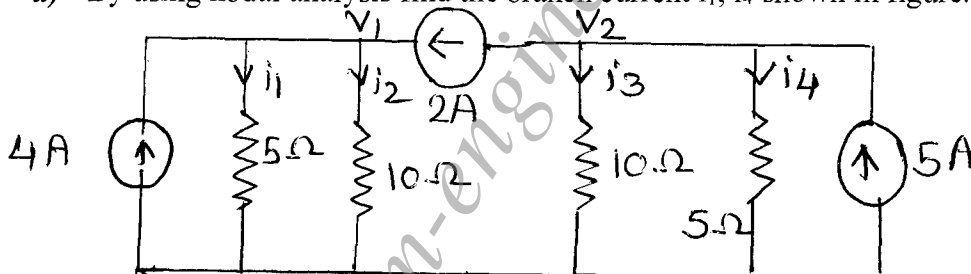
a) By using nodal analysis find the branch current i_1, i_4 shown in figure. **[05]**



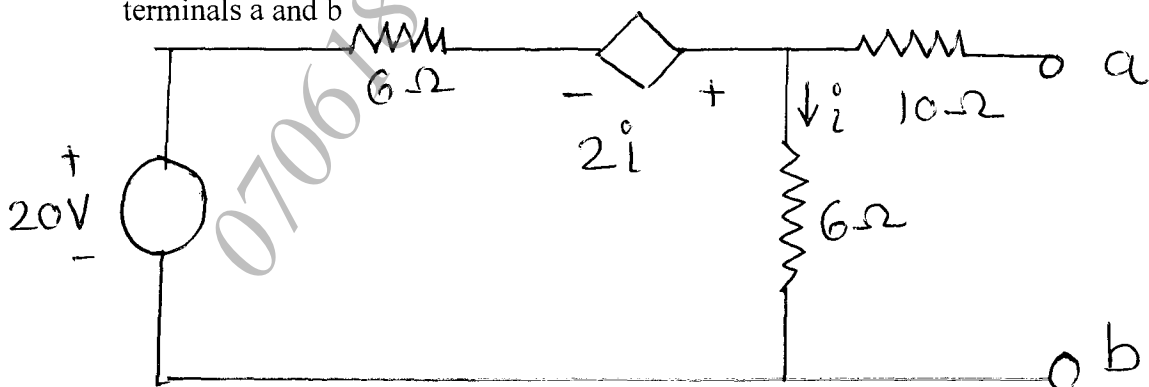b) Find the Thevenin's equivalent for the circuit shown in figure with respect to terminals a and b. **[05]**



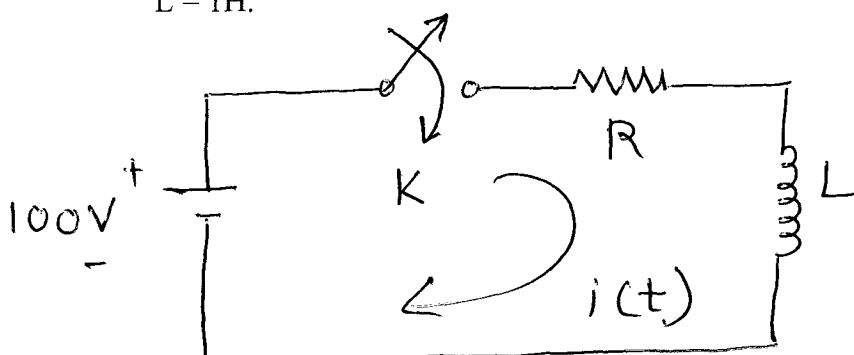Q.2 a) In the network of figure. If $t = 0$, switch 'k' is closed. Find the value of $i, di/dt$ and d^2i/dt^2 at $t = 0^+$ for element values as follows: $V = 100\text{ V}$, $R = 1000\ \Omega$ and $L = 1\text{ H}$. **[05]**




P.T.O.


- b) A series R-C circuit with initial current I_0 in the capacitor is connected to a d.c. voltage V at $t = 0$. Derive expression for the instantaneous current through the capacitor for $t > 0$. [05]

OR

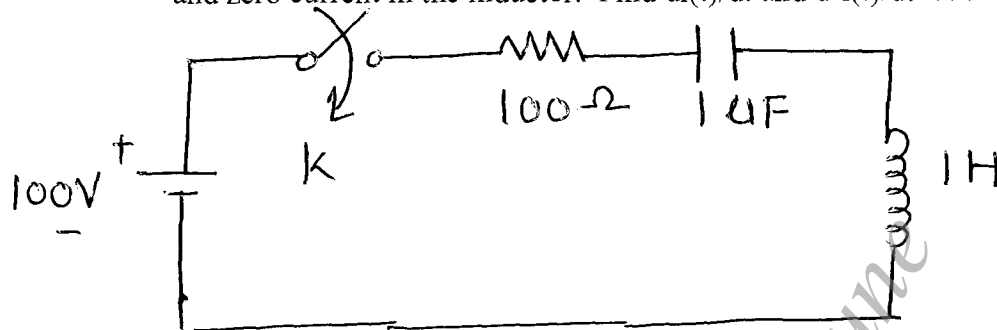- a) What is the significance of initial conditions? Write a note on initial conditions in basic circuit. [05]
- b) In the given circuit figure switch 'K' is closed at $t = 0$ with capacitor uncharged and zero current in the inductor. Find $di(t)/dt$ and $d^2i(t)/dt^2$ at $t = 0$. [05]



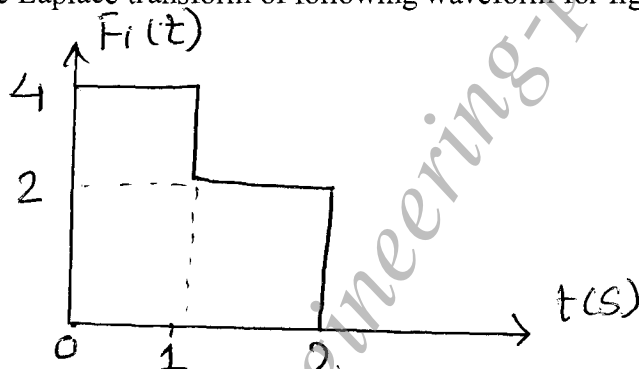- Q.3 a) Find the Laplace transform of following waveform for figure. [05]



- b) Define and explain the characteristics of: [05]
- Unit step function
 - Unit ramp function
 - Unit impulse function

OR

- a) State any three properties of Laplace transform. [05]
- b) State and explain time displacement theorem and convolution theorem. [05]

- Q.4 a) Express Transmission parameters in terms of Z parameters. [05]


- b) State and explain the method to calculate driving point impedance at port 1 with port 2 open. [05]

OR

- a) Express Hybrid parameters in terms of Y parameters. [05]
- b) Draw the equivalent circuit of the hybrid parameter representation. [05]

Q.5 a) $Y(s) = \frac{25}{(s+4)(s^2+2s+2)}$. Obtain pole zero diagram. [05]

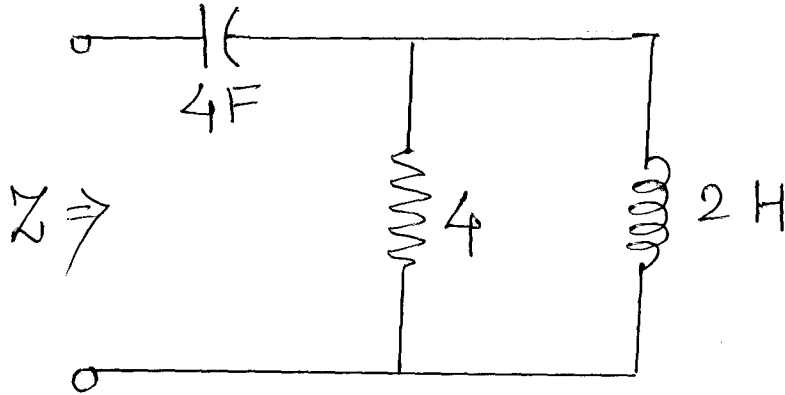
b) Find $z(s)$ for following network. [05]



OR

a) What are the necessary conditions for a transfer function? [05]

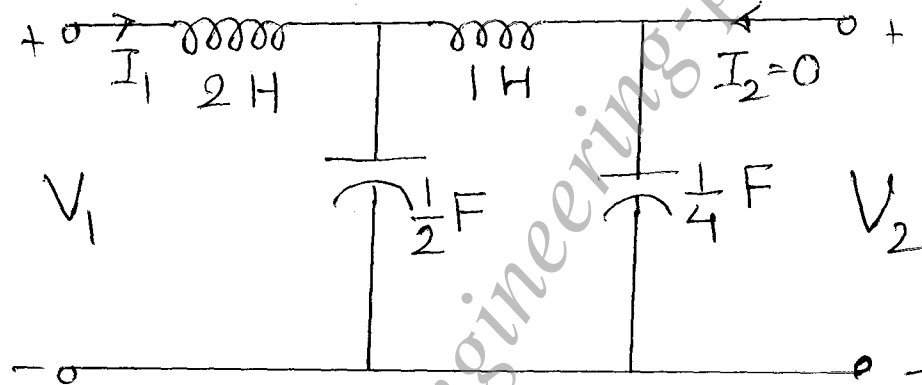b) Find driving point input impedance of ladder network. [05]



Q.6 a) Explain the following: [05]

- Odd function symmetry
- Trigonometric form of Fourier series

b) Obtain the coefficients of exponential Fourier series for the wave form. [05]



a) Obtain the Fourier expansion in exponential form for the square wave defined [05]

$$f(t) = \begin{cases} 1, & 0 < t < T/2 \\ -1, & T/2 < t < T \end{cases}$$

b) Find trigonometric Fourier series of the wave form. [05]

