

B. TECH. SEM -III (E & TC ENGG.) (2014 COURSE) (CBCS) :

SUMMER - 2018

SUBJECT : NETWORK THEORY

Day : **Friday**
Date : **25/05/2018**


S-2018-2269

Time : **02.30 PM TO 05.30 PM**
Max. Marks : 60


N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Use of non-programmable **CALCULATOR** is allowed.
- 4) Draw neat and labeled diagram **WHEREVER** necessary.
- 5) Assume suitable data if necessary.

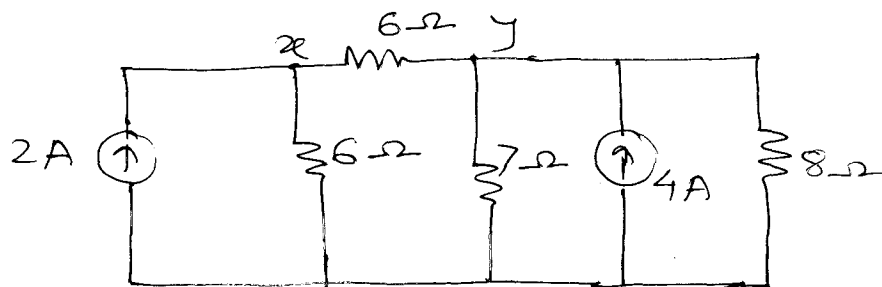Q.1 a) Using nodal method find voltage V_{xy} for the shown network. **[05]**




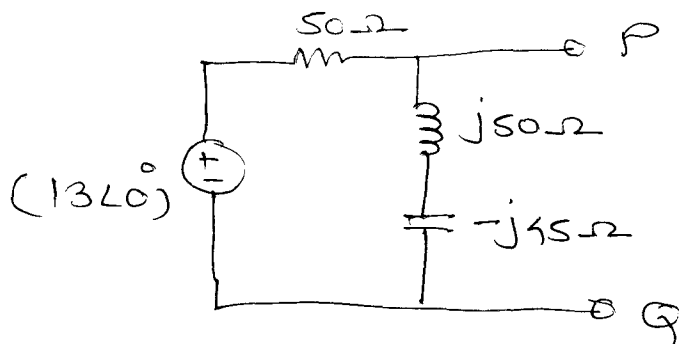b) Find load impedance required to be connected across the terminals P – Q for the maximum power transfer in the shown network. Also find maximum power delivered to the load. **[05]**




OR

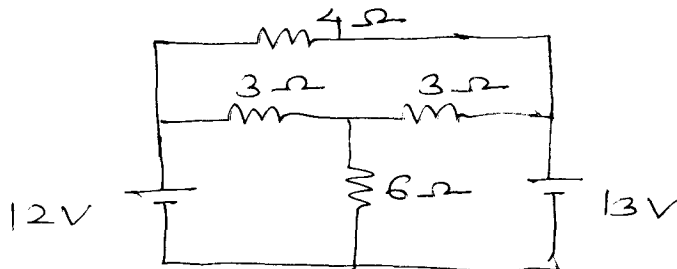a) Write loop current equations for the shown network and determine current through 6Ω resistor. **[05]**




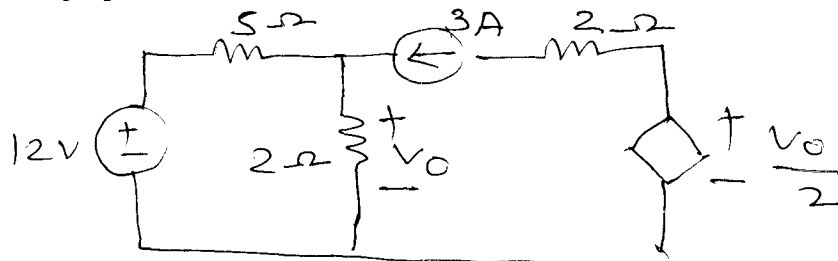b) Using superposition find V_0 of the shown network. **[05]**



P.T.O.

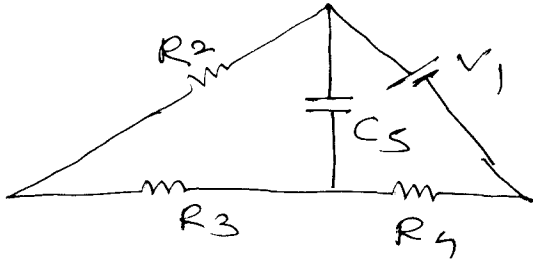
- Q.2 a) Consider the network shown in figure. Determine the branch current in terms of loop current for the tree of your choice. [06]




- b) Define rank of all matrices. [04]

OR

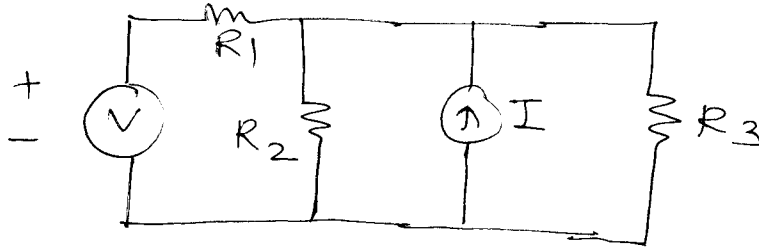- a) For the shown network find graph and indicate the number of all possible trees for that graph. [05]




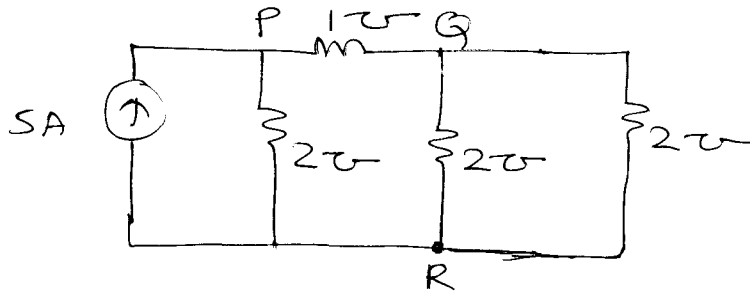- b) For the shown network find out f-cutsets and for f-cutset matrix. [05]



- Q.3 a) Find out unit step response of series RL circuit using laplace transform. [05]

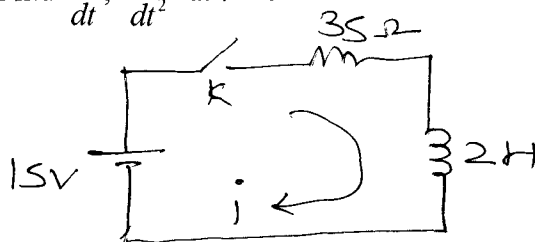- b) For the shown network switch is closed at $t = 0$ with the zero current in the inductor. Find $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$ [05]



OR

- a) Find out unit step response of series RC circuit using classical or laplace transform. [05]

- b) For the series R - C circuit $R = 45\Omega$ and $C = 0.3F$. Initially switch is open for long time. At $t = 0$ it is closed. Find expression for $V_C(t)$ and $V_R(t)$ against time. [05]

...3...

- Q.4 a) Derive quality factor when single inductor is connected in circuit. [05]
b) What is the effect of $f = f_r$, $f > f_r$ and $f < f_r$ on resonant circuit? [05]

OR

- a) Derive quality factor when single capacitor is connected in circuit. [05]
b) Draw and explain various impedance curves for series RLC circuit. [05]

- Q.5 a) Enlist the electrical characteristics of passive filter? Explain any one in detail. [05]
b) Design constant K – LPF T and π section filters to be terminated in 600Ω resistance. The cut-off frequency is 3KHz. [05]

OR

- a) Derive design formulas of K-prototype low pass filter. [05]
b) Design m derived LPF T section filter to be terminated in 620Ω resistance. Cut off frequency is 1.8KHz and infinite attenuation occurs at 2KHz. [05]


- Q.6 a) Find out condition for reciprocity and symmetry for two port network in terms of short circuit admittance parameters. [05]

- b) Prove that for cascade connection of two networks. [05]

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

OR

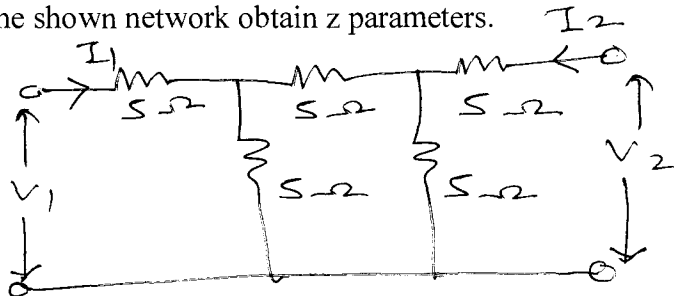- a) For the shown network obtain z parameters. [05]



- b) Find hybrid parameters in terms of Y parameters. [05]

* * * *