

F.Y. B. SC. (Computer Science) SEM – I (2014 COURSE) : WINTER
2018

SUBJECT: LINEAR ELECTRONICS – I

Day: - Saturday
Date: 20/10/2018

W-2018-0942

Time: 12.00 NOON TO 02.00 PM
Max. Marks: 40

N.B.:


- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw diagrams **WHEREVER** necessary.
- 4) Use of scientific **CALCULATOR** is allowed.

Q.1 Answer any **TWO** of the following: (10)

- a) Explain the working of n – channel enhancement MOSFET with neat diagram.
- b) i) Give the colour code theory to calculate the values of fixed resistors.
ii) Find the colour bands of resistors if its value is : $100\text{ K } \Omega \pm 10\%$ and $4.7\text{K } \Omega \pm 5\%$.
- c) Classify the amplifiers on the basis of operating point with necessary diagram for each.

Q.2 Answer any **TWO** of the following: (10)

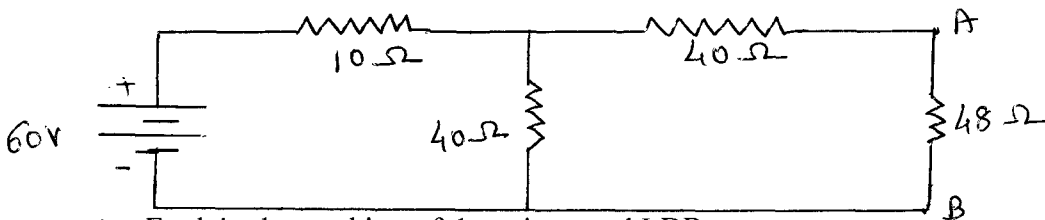
- a) Draw a neat labeled circuit diagram of single stage RC coupled CE- amplifier. Explain the role of coupling and emitter bypass capacitor. Also give the expression for voltage gain of this amplifier.
- b) Find the current through the load using Norton's theorem.



- c) Explain the working of thermistor and LDR.

Q.3 Answer any **TWO** of the following: (10)

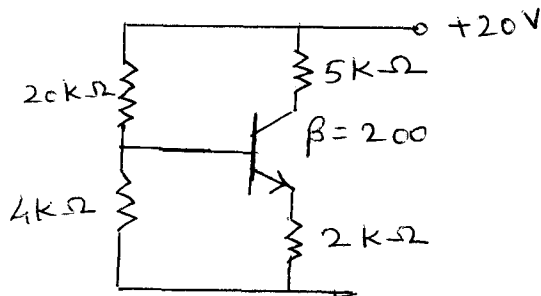- a) With necessary diagram explain the working principle of SCR.
- b) Draw dc load line for the following circuit.



- c) Obtain equations for growth and decay of current in LR circuit.

Q.4 Answer any **FIVE** of the following: (10)

- a) In a transformer number of turns in primary $N_p=100$, number of turns in secondary $N_s = 200$. If voltage applied to primary $V_p = 200\text{V}$. Find the secondary voltage V_s .
- b) Draw symbols for the following:
i) UJT ii) LDR
- c) Define the following terms for resistor :power rating and tolerance.
- d) Give two points of difference between FET and MOSFET.
- e) State maximum power transfer theorem.
- f) Define inductance. State its types.
- g) Draw well-labeled diagram for CB- configuration of transistor.