

S.Y.B.SC. SEM – IV (CBCS - 2016 Course) : WINTER - 2018
SUBJECT : PHYSICS : ELECTRONICS

Day : Friday
Date : 19/10/2018

W-2018-0728

Time : 03.00 P.M. To 06.00 P.M
Max. Marks : 60

N. B. :


- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Use of **SCIENTIFIC** calculator is allowed.

Q.1 Answer **ANY TWO** of the following: (12)

- a) With necessary diagram explain the output characteristic of transistor in CE – mode.
- b) State and explain De-Morgan's first and second theorem.
- c) Explain the construction and working principle of UJT.

Q.2 Answer **ANY TWO** of the following: (12)

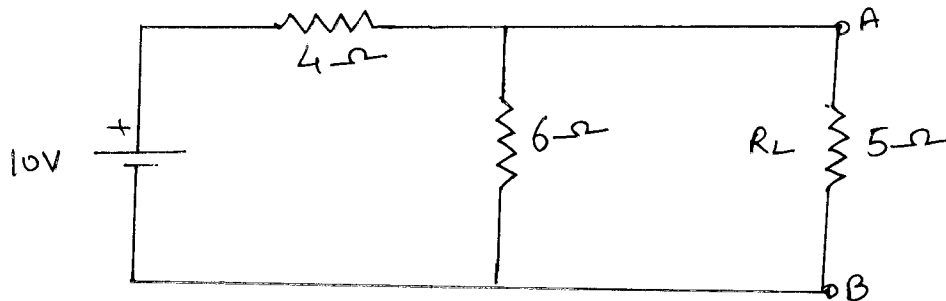- a) What is a flip-flop? Explain the working of RS-flip-flop with NAND gates and truth table.
- b) Explain the potential divider bias method for transistors.
- c) i) Give statement for Norton's theorem. ii) Nortanize the following circuit.



Q.3 Answer **ANY TWO** of the following: (12)

- a) Explain the following gates with respect to symbol and truth table:
i) EXOR ii) NOR iii) AND
- b) With neat diagram explain the action of full wave rectifier.
- c) Explain the block diagram of amplifier with feedback.

Q.4 Answer **ANY THREE** of the following: (12)

- a) Convert the following:
i) $(11011110:101)_2 = (?)_{10}$ ii) $(3A9E. BOD)_{16} = (?)_2$
- b) Explain the types of multivibrator.
- c) Draw block diagram of SMPS and explain the function of each block.
- d) Explain the input characteristic of transistor in CB mode.

Q.5 Answer **ANY FOUR** of the following: (12)

- a) Draw neat diagrams for the transistor in CB and CE configuration.
- b) For a certain transistor in CE configuration, $\alpha = 0.98$. If $I_E = 25$ mA, determine I_B and I_C
- c) i) Add using 2's complement -75 to $+26$
ii) Using 2's complement, subtract 101 from 111.
- d) Explain the concept of ERPS.
- e) State any three Boolean laws.
- f) Explain the three pin regulator IC7805

* * * * *