

**F.Y. B. SC. (Computer Science) SEM –II (CBCS - 2016 COURSE) :**  
**WINTER - 2018**

**SUBJECT : PRINCIPLES OF DIGITAL ELECTRONICS -II**

Day : Saturday  
Date : 27/10/2018

**W-2018-0911**

Time : 03.00 PM TO 06.00 PM  
Max. Marks : 60

---

**N. B. :**

- 1) All Questions are **COMPULSORY**
  - 2) Figures to the right indicate **FULL** marks.
  - 3) Use of scientific calculator is **ALLOWED**.
- 

**Q.1 A) Select the correct option and rewrite the complete sentence. (06)**

a) The number of states counted by MOD-10 counter are \_\_\_\_\_.

- |        |        |
|--------|--------|
| i) 5   | ii) 10 |
| iii) 8 | iv) 6  |

b) Full form of SIPO is \_\_\_\_\_.

- |                                 |                                |
|---------------------------------|--------------------------------|
| i) Serial –in–parallel –out     | ii) Sustain –in parallel – out |
| iii) Simplify –in–parallel –out | iv) Serially –in–Process –out  |

c) One shot multivibrator is also known as \_\_\_\_\_ multivibrator

- |                 |                   |
|-----------------|-------------------|
| i) Bistable     | ii) Astable       |
| iii) Monostable | iv) None of these |

d) The terminal count for a 4-bit counter in up mode is \_\_\_\_\_.

- |           |          |
|-----------|----------|
| i) 1111   | ii) 1010 |
| iii) 0000 | iv) 1110 |

e) The condition for J-K flip-Flop to toggle is \_\_\_\_\_.

- |               |              |
|---------------|--------------|
| i) J=1, K=0   | ii) J=0, K=0 |
| iii) J=1, K=1 | iv) J=0, K=1 |

f) EPROM stands for \_\_\_\_\_.

- i) Electrically Programmable Read Only Memory
- ii) Erasable Peripheral Read Only Memory
- iii) Erasable Programmable Read Only Memory
- iv) Electrical Peripheral Read Only Memory

**B) Answer the questions in one sentence. (06)**

- a) Draw symbol for D flip-flop.
- b) What is the function of clear input in flip-flop.
- c) State the types of shift registers.
- d) Write any two application of astable multivibrator.
- e) State the limitation of static RAM.
- f) What is race around condition in JK flip – flop.

- Q.2** Answer any **THREE** of the following. (12)
- Explain the concept of Static RAM and Dynamic RAM
  - Write a note on 4 bit PIPO shift register
  - Define modulus of a counter. Explain the action of MOD-10 counter using IC 7490
  - Explain the concept of asynchronous counter and synchronous counter.
- Q.3** Answer any **FOUR** of the following . (12)
- Explain any three applications of ROM
  - A timer 555 is configured to turn in as table mode with  $R_s = 4k\Omega$  and  $R_B = 4k\Omega$   $C = 0.01 \mu F$ . Determine the frequency of the output and duty cycle
  - With necessary diagram explain the action of ring counter.
  - Draw diagram for a asynchronous up-down counter.
  - Give the classification of memory.
- Q.4** Answer any **TWO** of the following . (12)
- Explain the action of 4 bit shift register in serial –in-serial-out mode.
  - Explain the working of IC555 as bistable multivibrator .
  - Using NOR gates explain the action of RS flip-flop.
- Q.5** Answer any **TWO** of the following. (12)
- Explain the action of 3 bit down counter using logic diagram, waveform and truth table
  - Construct the following counters using IC 7490:
    - MOD 3
    - MOD 5
  - Explain the action of JK master slave Flip-Flop with neat diagram.

\* \* \* \* \*