

SUBJECT : ANALOG ELECTRONICS

Day : Monday
Date : 26/11/2018

W-2018-2301

Time : 10.00 AM TO 01.00 PM
Max. Marks : 60

N. B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Assume suitable data, if necessary.

Q.1 a) Design a fixed bias circuit for CE amplifier such that an operating point is $V_{CE}=8V$ and $I_C=2mA$, supply voltage is $15V$ with silicon transistor of $\beta=100$. Consider emitter base voltage is $0.6V$. Calculate value of base resistor and load resistor that would be employed. (06)

b) Discuss requirements of biasing circuits. (04)

OR


a) Discuss Thermal runaway process in detail with diagram. (06)

b) Derive general expression for stability factor. (04)

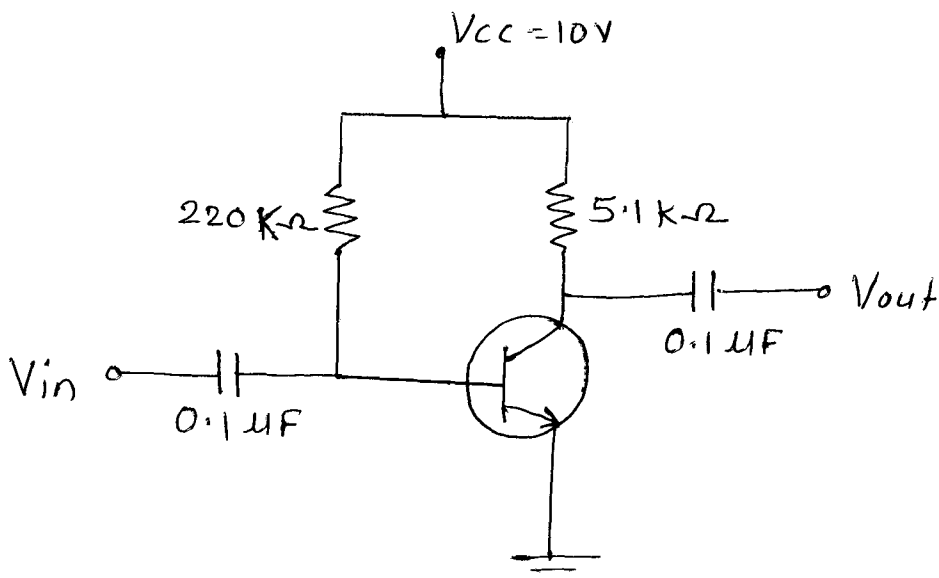Q.2 Consider a single stage Common Collector amplifier with $R_S=1K\Omega$, $R_L=1.2K\Omega$.
If $h_{ie}=1.1K$, $h_{re}=2.5 \times 10^{-4}$, $h_{fe}=50$ and $h_{oe}=25\mu A/V$
Calculate $-A_v$, A_{VS} , A_P and R_O (10)

OR

Determine input impedance, output impedance, voltage gain and current gain for CE Amplifier shown in Figure. The h-Parameters of transistor are $h_{fe}=60$, $h_{ie}=500\Omega$ at $I_C=3mA$




P. T. O.

- Q.3 a)** Discuss in detail following JFET parameters: (10)
- Drain resistance
 - Transconductance
 - Amplification Factor

Derive the relation between above parameters.

OR

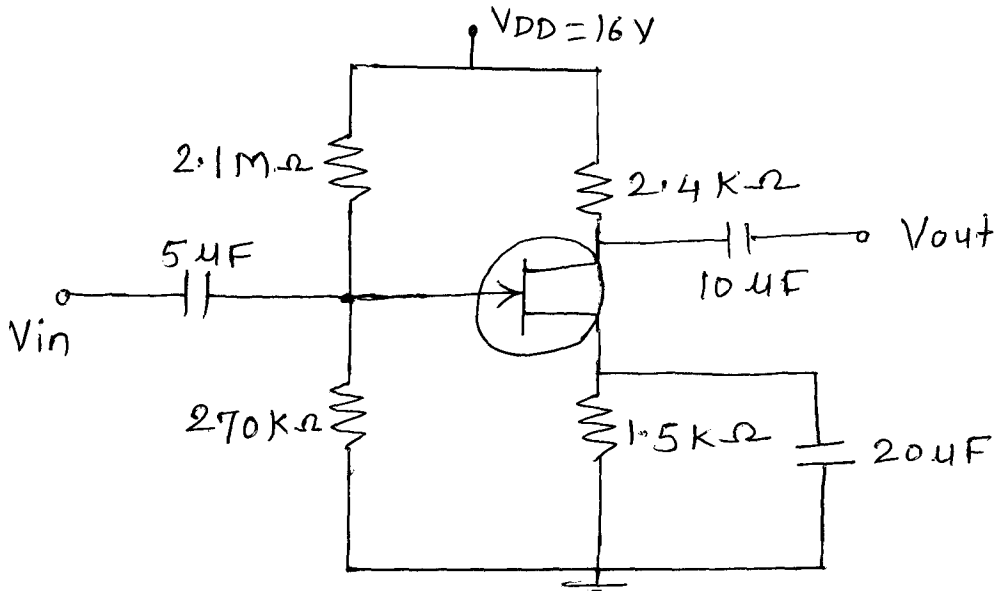For voltage divider JFET circuit, Find the values of V_D , V_S , V_{DS} , V_{DG}
For $I_D=2.4\text{mA}$, $V_{GS}=-1.8\text{V}$



- Q.4** Discuss the operation of n-channel Depletion MOSFET with Negative V_{GS} and positive V_{GS} . Draw the transfer characteristics for the same. (10)

OR

Describe the situation when pinch-off occurs in n-channel enhancement MOSFET when positive V_{DS} voltage is applied. Draw the transfer characteristic graph.

- Q.5** Discuss the operation of simple and biased positive and negative clipper circuits with input and output waveforms. (10)

OR

- Draw and explain operation of voltage quadrupler circuit (06)
- Draw any one type of multivibrator circuit with waveforms (04)

- Q.6 a)** What is photodiode? Why photodiode is always used in reverse biased condition? (06)

- Discuss the operation of photovoltaic cell (04)

OR

Describe the rules for preparing artwork in PCB designing process in detail. (10)

* * * * *