

**B. Tech. Sem – III (Biomedical Engg.) (2014 COURSE) (CBCS) :
WINTER - 2018**

SUBJECT: CIRCUIT THEORY

Day : Friday
Date : 30/11/2018


Time : 10.00 AM TO 01.00 PM
Max. Marks: 60.

W-2018-2321

N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate full marks.
- 3) Draw neat labeled diagrams **WHEREVER** necessary.

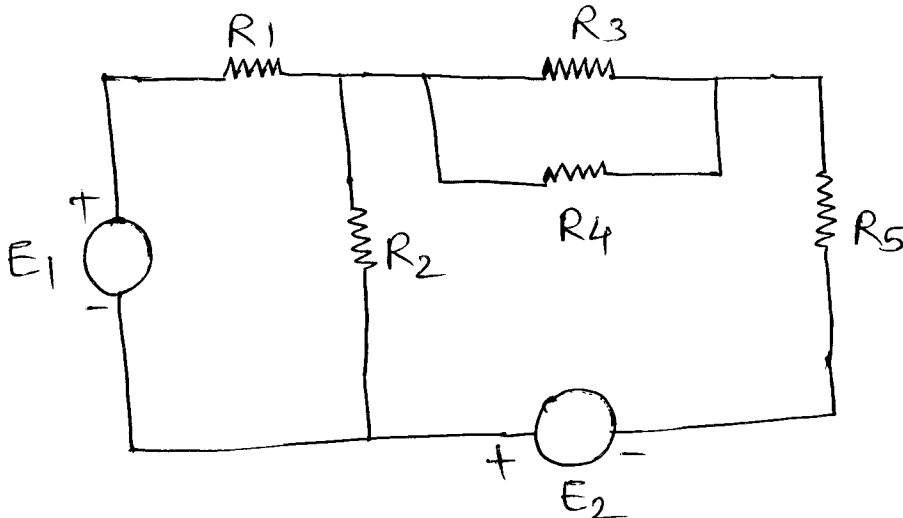Q.1 Find the current through R_2 using superposition theorem for the following figure. (10)




$$\begin{aligned}
 E_1 &= E_2 = 100 \text{ V} \\
 R_1 &= 40 \text{ } \Omega \\
 R_2 &= 20 \text{ } \Omega \\
 R_3 &= 5 \text{ } \Omega \\
 R_4 &= 20 \text{ } \Omega \\
 R_5 &= 16 \text{ } \Omega
 \end{aligned}$$

OR

State and explain Norton's and Maximum power transfer theorem. (10)

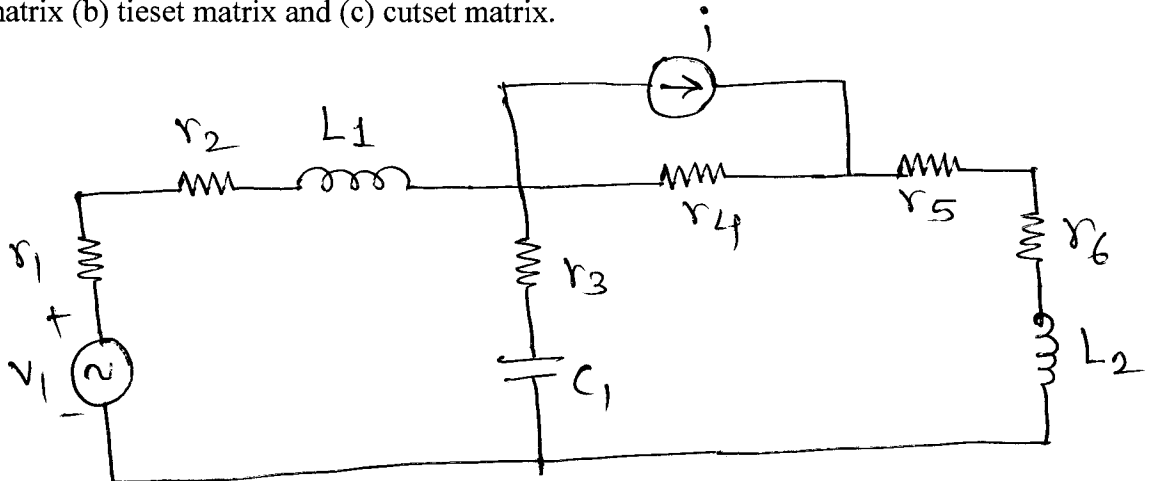Q.2 For the circuit shown in figure, draw the oriented graph and write (a) incidence matrix (b) tieset matrix and (c) cutset matrix. (10)



OR


Define the following terms with examples. (10)
(i) Planar graph (ii) Tree (iii) Co-tree (iv) Path (v) Loop.

Q.3 Derive the expressions for driven and undriven RL circuit. (10)

OR

P.T.O.

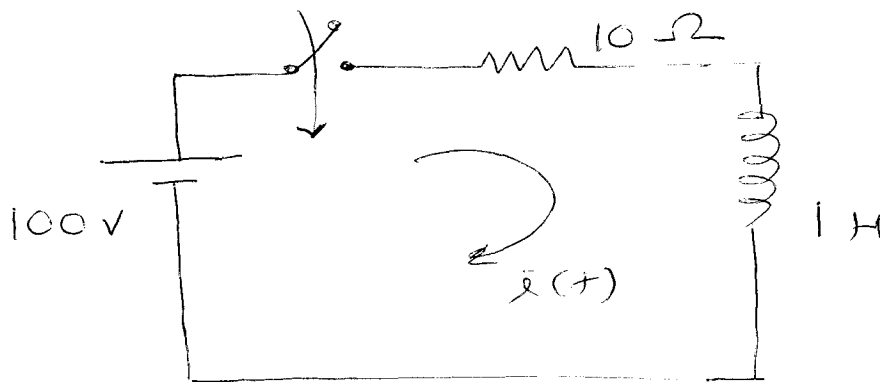In the network shown in the figure, the switch is closed at $t=0$, with zero current in the inductor, find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$. (10)



Q.4 For series resonant circuit, derive the following expressions- (10)
 (i) Resonant frequency (ii) Q-factor (iii) Bandwidth.

OR

A $50\ \mu\text{F}$ capacitor, in series with a coil having $4\ \Omega$ resistance, resonates at 1 kHz. (10)
 Find the inductance of the coil. Also find the circuit current if the applied voltage is 10V.

Q.5 a) Explain the working of constant-k high pass filter with impedance curves and (05)
 derive the expression for cut-off frequency.
 b) Compare m-derived filter and prototype filter. (05)

OR

Design a constant-k low pass filter to match with a line having characteristic (10)
 impedance of $500\ \Omega$ and to pass frequencies up to 5 kHz.

Q.6 Derive the expressions for reciprocity and symmetry conditions in terms of Y and (10)
 H-parameters.

OR

The Z-parameters of a two port network are (10)
 $Z_{11} = 20\ \Omega$, $Z_{22} = 30\ \Omega$, $Z_{12} = Z_{21} = 10\ \Omega$. Find Y and ABCD parameters.

* * *