

**B. Tech. Sem -III (E & TC Engg.) (2014 COURSE) (CBCS) :**  
**WINTER - 2018**

**SUBJECT: DIGITAL CIRCUITS & APPLICATIONS**

Day: Friday  
Date: 30/11/2018

Time: 10.00 AM TO 01.00 PM  
Max Marks. 60

**W-2018-2324**

**N.B.:**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks
- 3) Draw the labeled diagrams **WHEREVER** necessary

**Q.1 a)** What is BCD code? Explain the rules for BCD addition with one example **(04)**

**b)** Minimize the logic function using K map and draw logic diagram **(06)**  
 $f(A,B,C,D)=\sum m(0,1,2,3,5,7,8,9,11,14)$

**OR**

**a)** Convert following decimal numbers into it's equivalent binary numbers **(05)**  
I.(25.75)<sub>10</sub> II.(115)<sub>10</sub>

**b)** What are Demorgan's theorems? Write them in equation form, prepare their truth tables to prove their correctness **(05)**

**Q.2 a)** Draw 4-bit parallel adder diagram using full adder. **(05)**

**b)** What is Priority encoder? **(05)**

**OR**

**a)** What is comparator? Explain 2 bit magnitude comparator **(05)**

**b)** What is code converter? Explain any type of code converter **(05)**

**Q.3 a)** What are the characteristics of digital ICs and families? Explain **(05)**

**b)** Draw And explain the operation of CMOS NOR gate **(05)**

**OR**

**a)** Design and explain standard TTL with open collector output configuration **(05)**

**b)** Draw And explain the operation of CMOS NAND gate **(05)**

**Q.4 a)** What is the difference between latch and flip flop **(03)**

**b)** Reduce the number of states in the following state tables and draw state diagram for it **(07)**

Present state	Next state		Output	
	X=0	X=1	X=0	X=1
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

P.T.O.

**OR**

- a) Design T flip flop using J-K flip flop (05)
- b) What is state machine? Explain Mealy and Moore state machines with examples (05)

- Q.5** a) What are types of shift registers? Explain anyone in detail (05)
- b) Design 4 bit Asynchronous up counter (05)

**OR**

- a) What is the difference between Synchronous and Asynchronous counter? (05)
- b) Design 4 bit Ring counter. (05)

- Q.6** a) A combinational circuit is defined by function (05)  
 $F_1 = \sum m (1,5,7, 9,11,12)$   
 $F_2 = \sum m (5,6,7,10,11,13,15)$   
Implement the circuit with PLA

- b) Draw and explain structure of SRAM (05)

**OR**

- a) Implement full adder using PROM (05)
- b) Draw and explain structure of DRAM (05)

• \* \* \* \*