

B.Tech Sem – IV (2007 Course) (Electronics) : WINTER - 2018

SUBJECT: ELECTRONIC CIRCUITS

Day : Tuesday
Date : 13/11/2018

W-2018-2758

Time : 02.30 PM TO 05.30 PM
Max. Marks: 80

N. B.:

- 1) **Q.No.1 and Q.No.5 are COMPULSORY.** Out of the remaining attempt **ANY TWO** questions from each Section.
- 2) Figures to the right indicate **FULL** marks.
- 3) Answer to both the sections should be written in **SEPARATE** answer book.
- 4) Use of non-programmable electronic **CALCULATOR** is allowed.
- 5) Assume suitable data if necessary.

SECTION-I

- Q.1** a) Compare frequency response of RC coupled amplifier and direct coupled amplifier. (05)
b) What are the advantages of negative feedback amplifier? (05)
c) Draw the symbol of op-amp and state the significance of each terminal. (04)
- Q.2** a) Discuss the choice of the transistor configuration in a cascade amplifier. (06)
b) State various techniques used for improving the input impedance for CC stage and describe one in detail. (07)
- Q.3** a) What is the effect of employing negative feedback on input resistance and output resistance of a voltage series feedback amplifier? Write the derivation for it. (07)
b) If an amplifier with lower 3dB frequency f_L , upper 3dB frequency f_H and mid frequency gain A_{mid} is used in feedback application with feedback factor β , show that lower 3dB frequency of feedback amplifier = $f_{Lf} = \frac{f_L}{1 + \beta A_{mid}}$
and upper 3dB frequency of feedback amplifier = $f_{Hf} = f_H (1 + \beta A_{mid})$. (06)
- Q.4** a) What are the methods of improving CMRR? Explain one method in detail. (07)
b) Explain the block diagram of internal structure of op-amp stating function of each block. (06)

SECTION-II

- Q.5** a) What is crossover distortion? Describe a method to minimize this distortion. (05)
b) With the help of circuit diagram explain zener diode as shunt voltage regulator. (05)
c) Write a function of resonance circuit in tuned amplifier. (04)
- Q.6** a) What are the different distortions occur in a power amplifier? Show that even harmonics are cancelled at the output of a push pull class B power amplifier. (07)
b) Determine the percentage of second harmonic distortion for an amplifier supplying 1W power to a 10K Ω load. Assume zero signal dc collector current of 40 mA and dc collector current with signal as 46mA. (06)
- Q.7** a) Describe foldback current limiting techniques. (06)
b) Explain with neat circuit diagram working of RC phase shift oscillator with three RC sections. (07)
- Q.8** a) Give the typical values of hybrid π parameters with model. (06)
b) The following transistor measurements are made at $I_C = 5\text{mA}$ and $V_{CE} = 10\text{V}$ and at room temperature, $h_{fe} = 100$, $h_{ie} = 600 \Omega$, $|A_i| = 10$ at 10 MHz and $C_C = 3\text{pF}$. Find f_{β} , f_T , $r_{b'e}$ and $r_{bb'}$. (07)