


N. B. :

- 1) Q. No. 1 and Q. No. 5 are **COMPULSORY**. Out of remaining attempt **ANY TWO** questions from each section.
- 2) Figures to the right indicate **FULL** marks.
- 3) Answers to both the sections should be written in the **SEPARATE** answer books.
- 4) Draw neat and labeled diagram **WHEREVER** necessary.
- 5) Assume suitable data, if necessary.

SECTION - I

- Q. 1 a) State and explain Maximum power transfer theorem. (05)
- b) If $v = V_m \sin \omega t$ is applied across single phase circuit and current flowing through the circuit is $i = I_m \sin (\omega t + \phi)$. Derive the expression for average power consumed in the circuit. (05)
- c) Define and explain the terms MMF, Flux density, Field intensity, Permeability, Reluctance. (04)

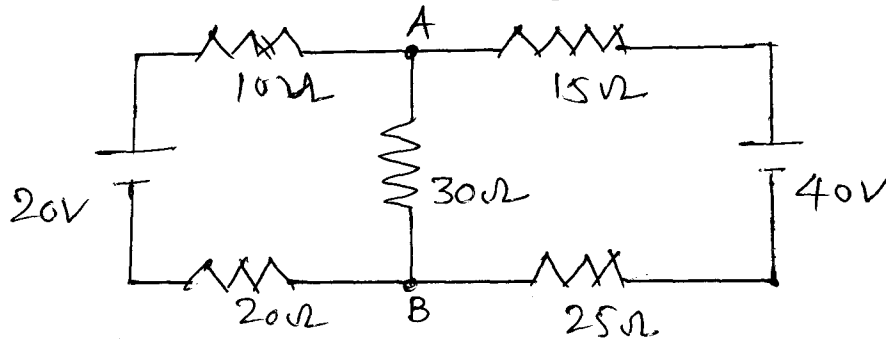- Q. 2 a) State and explain Kirchoff's law. (07)
- b) Using superposition theorem find the current flowing through the resistance connected between A-B, as shown in the fig (06)



- Q. 3 a) Explain the terms: (07)
- i) Symmetrical system
 - ii) Phase sequence
 - iii) Balanced load as related with three-phase system
- b) A load of 35 kw operated at 0.8 p.f. lagging when connected to 400V $1\phi, 50\text{Hz}$ source. (06)
- Find:
- i) Current in the load
 - ii) Power factor angle
 - iii) Impedance
 - iv) Resistance of load
 - v) Reactance of load

- Q. 4** a) A 20 kVA, 50 Hz, Single Phase Transformer has the iron loss and full load copper loss of 150 and 250 watts respectively. Find the efficiency of the transformer at (07)
- i) 40 % of full load at unity p.f.
 - ii) 50 % of full load at 0.8 lagging p.f.
- b) Compare electric and Magnetic circuit. (06)

SECTION – II

- Q. 5** a) Draw different waveforms related to full wave rectifier. (05)
- b) What are different types of resistors? Explain any one in brief. (05)
- c) Enlist salient features of Moving Iron instruments. (04)
- Q. 6** a) What are the first aid measures against Electric shock? (07)
- b) Draw schematic diagram of a power system showing voltage levels at each levels (generation, transmission, distribution) (06)
- Q. 7** a) Explain along with a neat block diagram, CRO. (07)
- b) Write a short note on Electrolytic Capacitors (06)
- Q. 8** a) Differentiate between Moving Coil and Moving Iron instruments. (07)
- b) Explain the working principle of single phase energy meter along with a suitable diagram. (06)

* * * * *