

B. Tech. Sem –III (Electrical Engg.) 2014 COURSE) (CBCS) :
WINTER - 2018

SUBJECT : LINEAR AND DIGITAL INTEGRATED CIRCUITS

Day: Wednesday
Date: 28/11/2018

W-2018-2298

Time: 10.00 AM TO 01.00 PM
Max. Marks:60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat diagrams **WHEREVER** necessary.

Q.1 a) Draw open loop and closed loop frequency response of operational amplifier and explain. State typical values of gain and bandwidth for an op amp 741. **(04)**

b) Define : **(06)**
i) Input offset voltage ii) Bias current iii) CMRR

OR

Q.1 a) Draw circuit diagram of noninverting ac amplifier with a gain of 101, with R_f & R_i values. If $v_{in} = 0.02\sin \omega t$, what is the output voltage? **(04)**

b) Draw circuit diagram of V to I converter and describe its operation. **(06)**

Q.2 a) Draw circuit diagram of op.amp as integrator and write mathematical equation. Draw input and output waveforms when square wave of 2V 1kHz is applied at input. **(05)**

b) Describe the operation of zero crossing detector with circuit diagram and input, output waveforms. **(05)**

OR

Q.2 a) Draw circuit diagram of precision full wave rectifier and describe its operation with input, output waveforms. **(05)**

b) Draw circuit diagram and explain sample and hold circuit. **(05)**

Q.3 a) What is the difference between passive filter and active filter? Draw circuit diagram and frequency response of first order low pass and high pass filter. **(06)**

b) State specifications of IC 723 and draw its pin diagram. **(04)**

OR

Q.3 a) Draw IC555 block diagram and describe its operation as astable multivibrator. Show output waveform and state frequency of operation. **(06)**

b) Draw three pin regulator diagram and state its specifications. **(04)**

Q.4 a) Convert the following: **(04)**

i) $(1E.53)_{16} = (___)_8$

ii) $(170)_{10} = (___)_{16}$

iii) $(0.345)_{10} = (___)_8$

iv) $(24)_8 = (___)_2$

b) Explain 1 bit comparator with neat block diagram & truth table. **(06)**

P.T.O.

OR

Q.4 State and prove the two D'Morgan's theorem with neat truth table. **(10)**

Q.5 a) Draw a neat labeled diagram of full adder using gates & explain the working using truth table. **(06)**

b) Why is NAND & NOR gate called as universal gate? Explain giving two examples each. **(04)**

OR

Q.5 a) Design BCD to 7 segment decoder with the help of truth table. Draw its logic diagram. **(07)**

b) Compare static RAM & Dynamic RAM. **(03)**

Q.6 a) Compare Asynchronous & synchronous counter. **(04)**

b) List various types of shift registers & explain each with the help of logic diagram. **(06)**

OR

Q.6 a) Draw the symbol & write the truth table of following : **(08)**
i) SR ii) JK iii) T iv) D

b) Explain D latch with the help of logic symbol & truth table. **(02)**

* * * * *