

B.Tech Sem – IV(2007 Course) (Electronics) : WINTER - 2018

SUBJECT: LINEAR INTEGRATED CIRCUITS

Day : Friday
Date : 16/11/2018

W-2018-2761

Time : 02.30 PM TO 05.30 PM
Max. Marks: 80

N. B. :

- 1) **Q. No.1 and Q. No. 5 are COMPULSORY.** Out of remaining attempt **Any TWO** questions from each section.
 - 2) Figures to the right indicate **FULL** marks.
 - 3) Answers to both the sections should be written in the **SEPARATE** answer book.
 - 4) Neat diagrams must be drawn **WHEREVER** necessary.
-

SECTION-I

- Q.1**
- a) Discuss the working of Widlar current source with neat circuit diagram. (05)
 - b) Draw the neat circuit diagram of an instrumentation amplifier using three OPAMP. (04)
 - c) Discuss the operation of peak detector using OPAMP. (05)
- Q.2**
- a) Define the term input offset voltage and how it will be nullify using internal and external compensation techniques for an OPAMP. (07)
 - b) Define following parameters of an OPAMP. Also state their ideal values. (06)
i) Input offset voltage ii) Bias current iii) Open loop gain
- Q.3**
- a) Draw circuit diagram of basic integrator. Derive its output equation and draw the output waveforms for sine and square wave input. (07)
 - b) Draw the circuit diagram of peaking amplifier and discuss its operation in detail. (06)
- Q.4**
- a) Discuss schmitt trigger circuit with different UTP and LTP levels and derive an expression for V_{LT} , V_{UT} and hysteresis. (07)
 - b) Compare schmitt trigger and comparator. (06)

SECTION-II

- Q.5**
- a) Draw a neat circuit diagram of a voltage divider circuit using multiplier IC and discuss its operation. (05)
 - b) Define following terms for PLL: (04)
i) Capture range ii) Lock range
 - c) State and explain any one application of V to I converter. (05)
- Q.6**
- a) With neat circuit diagram, discuss the working of an astable multivibrator using an OPAMP and derive the expression for its frequency. (07)
 - b) Draw pin diagram for IC 8038 and state the function of each pin in detail. (06)
- Q.7**
- a) Discuss frequency synthesizer using PLL with circuit diagram. (06)
 - b) Draw functional block diagram of IC 555 and state its applications. (07)
- Q.8**
- a) Explain with neat circuit diagram of V to I converter for floating load. (07)
 - b) Describe I to V converter application in photodiode detector. (06)

* * * * *