

Day: Thursday  
Date: 15/11/2018


W-2018-2344

Time: 02.30 PM TO 05.30 PM  
Max Marks. 60


N.B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Assume suitable data if **necessary**.
- 4) Use non-programmable **calculator** is allowed.

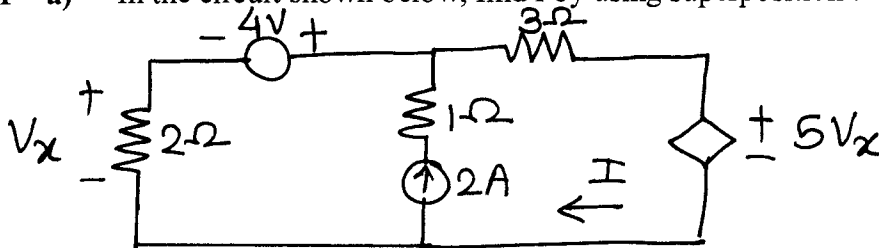Q.1 a) In the circuit shown below, find I by using superposition thm. (05)




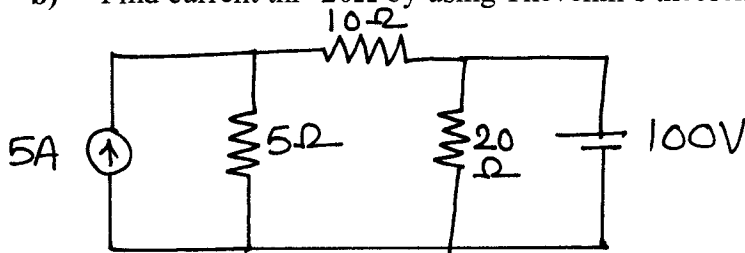b) Find current thr' 20Ω by using Thevenin's theorem. (05)




OR

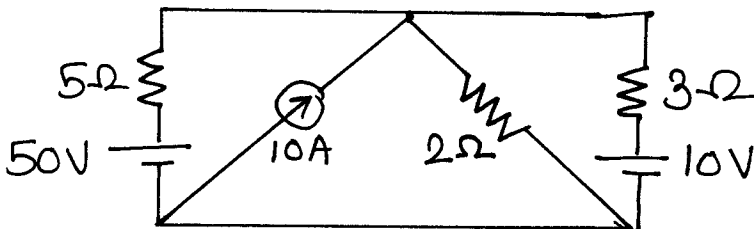Q.1 a) Find power delivered by 50V source in circuit using source transformation. (05)




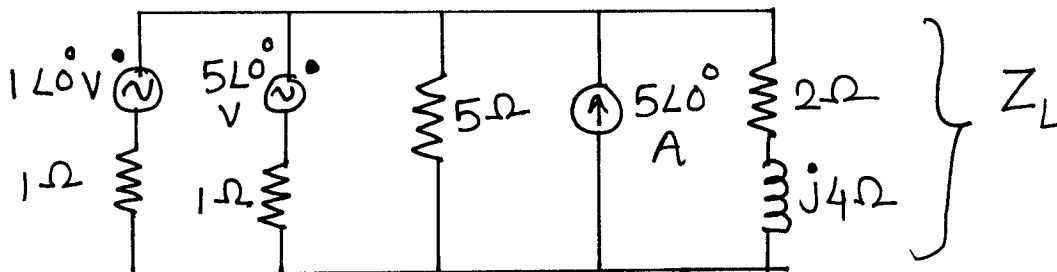b) Using Millmann's theorem. Find current in load  $Z_L$ .



Q.2 a) Determine the expression of current in series R-L circuit when it is excited by sinusoidal excitation. (05)

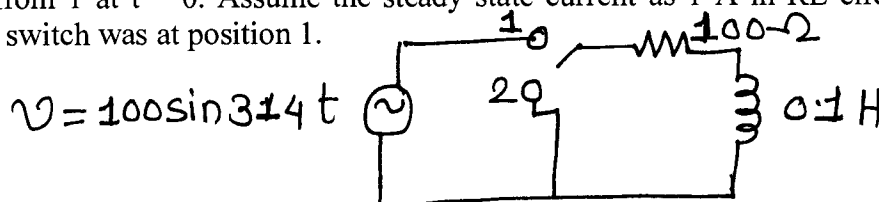
b) Obtain the current at  $t > 0$  if an ac voltage V is applied when switch is moved to 2 from 1 at  $t = 0$ . Assume the steady state current as 1 A in RL circuit when switch was at position 1. (05)



OR


Q.2 a) Derive the expression of current in series R-C circuit when it is excited by sinusoidal excitation. (05)

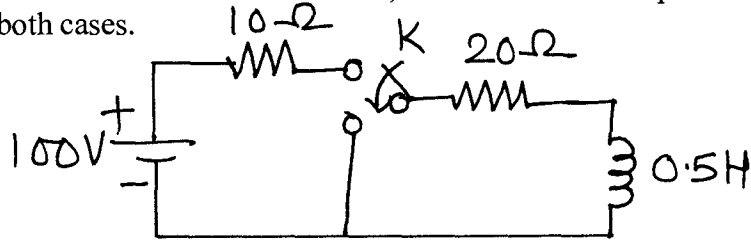b) In following circuit, the switch k is kept first at position 1 and steady state condition is achieved. At  $t = 0$ , switch is moved to position 2, find current in both cases. (05)




Q.3 a) Derive the expression of current in series R-L-C circuit when it is fed by step response. (05)

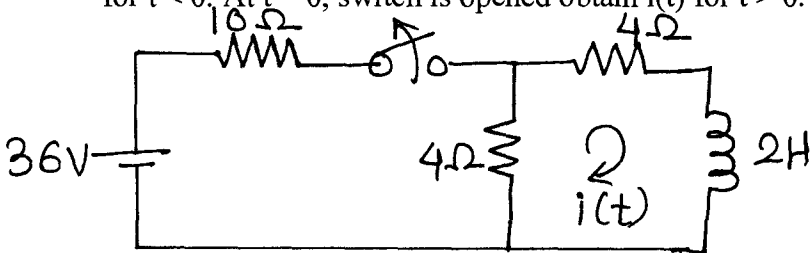b) The network shown in the figure has acquired steady state with switch closed for  $t < 0$ . At  $t = 0$ , switch is opened obtain  $i(t)$  for  $t > 0$ . (05)




OR

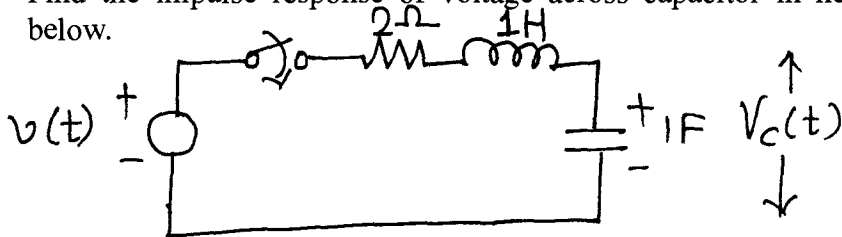
Q.3 a) Find the impulse response of voltage across capacitor in network shown below. (05)



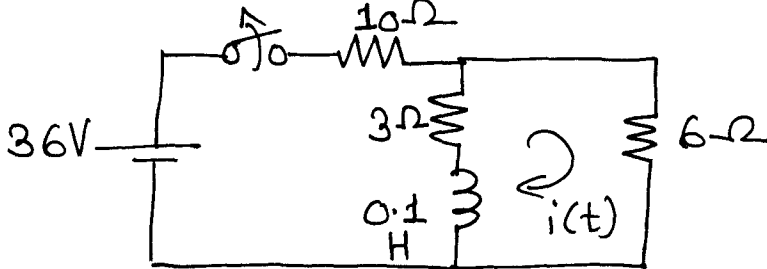b) Find  $i(t)$  if switch is open at  $t = 0$ , Use Laplace transform approach. (05)



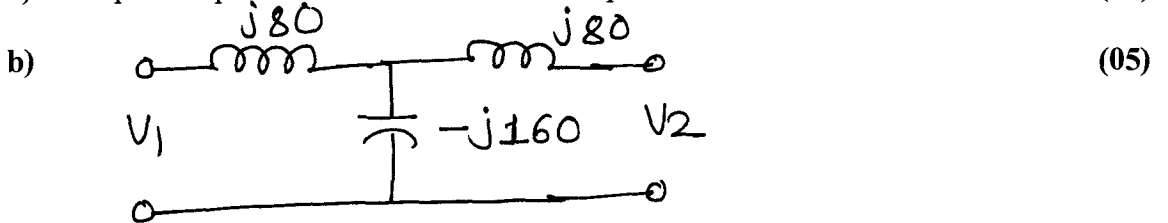Q.4 a) Express Z parameters in terms of ABCD parameters. (05)




Final Y and Z parameters.


OR

Q.4 a) Draw a neat labeled basic equivalent circuit for Y parameters. (05)

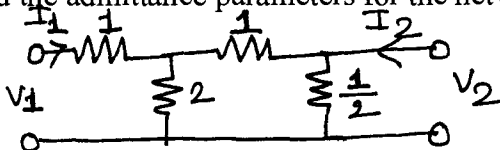b) Find the admittance parameters for the network. (05)



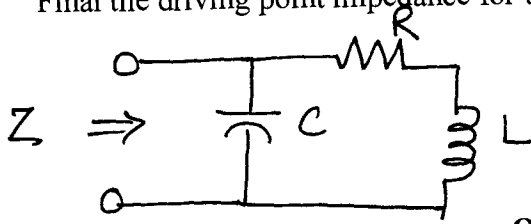- Q.5 a) Discuss the restrictions on poles and zeros for transfer function. (05)  
 b) Find the driving point impedance for the networks




OR

- Q.5 a) Obtain the pole zero plot for the following functions. (05)

$$H(s) = \frac{s^2 + 4}{s^2 + 6s + 4}$$


$$H(s) = \frac{5s - 12}{s^2 + 4s + 13}$$

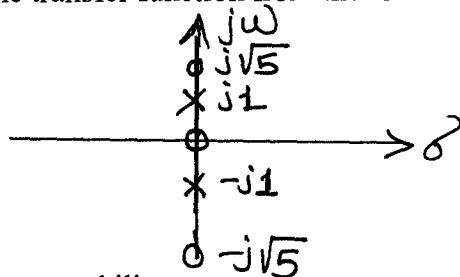- b) Obtain the transfer function from the following pole zero plot.




Comment on stability.

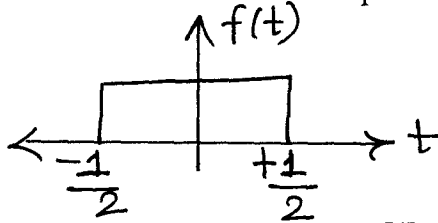- Q.6 a) State and explain the trigonometric form of Fourier series. (05)  
 b) Find the Fourier coefficient for the periodic signal.



OR

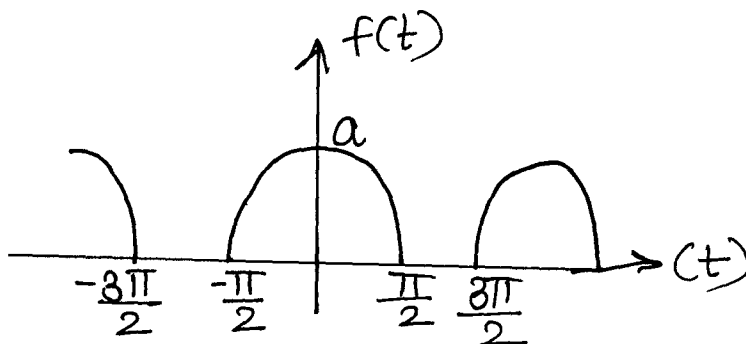- Q.6 a) Find the Fourier series of half wave rectified sine wave shown. (05)



- b) Define and explain in brief
- Even and odd symmetry
  - Half wave symmetry

\* \* \* \* \*