

B.Tech Sem – IV (2007 Course) (Electrical Engg.) : WINTER - 2018

SUBJECT: NETWORK ANALYSIS

Day: Thursday
Date: 15/11/2018

Time: 02.30 PM TO 05.30 PM
Max Marks. 80


W-2018-2755

N.B.


- 1) **Q. No. 1 & Q. No. 5 is COMPULSORY.** Out of remaining questions solve any **TWO** in each.
- 2) Figures to the right indicate **FULL** marks.
- 3) Both sections should be written in **SEPARATE** answer books.

SECTION – I

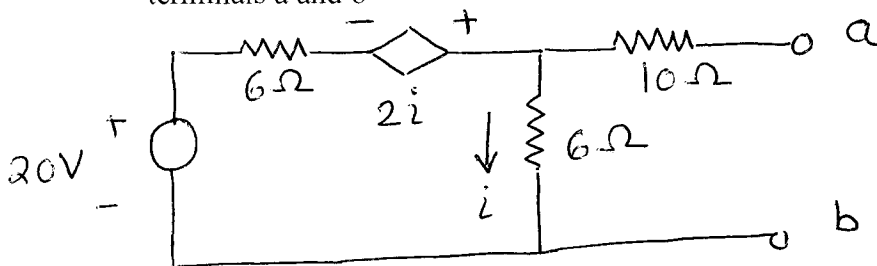
Q.1 a) Find the Thevenin's equivalent for the circuit shown as follow with respect to terminals a and b **(05)**



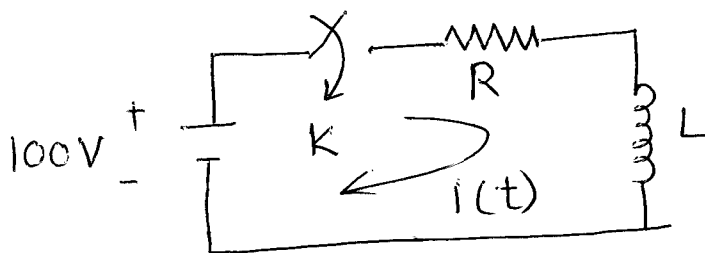b) In the network for figure shown below, at $t = 0$, switch 'k' is closed. Find the values of I , di/dt and d^2i/dt^2 at $t = 0^+$ for element values as follows; $V = 100V$, $R = 1000\Omega$ and $L = 1 H$ **(05)**




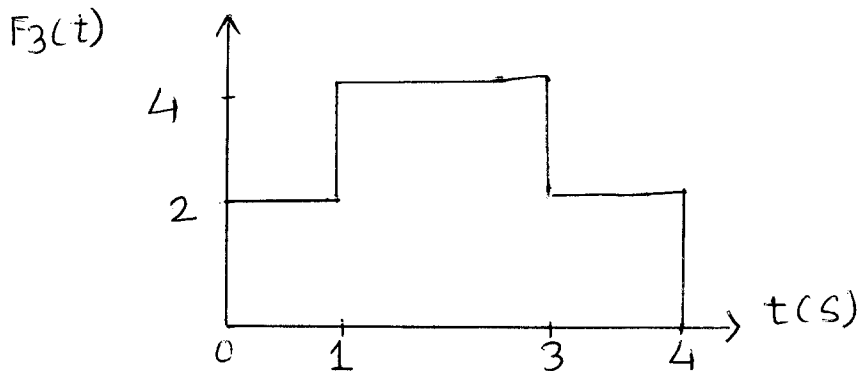c) Find Laplace transform of following waveform **(04)**




Q.2 a) State and explain reciprocity Theorem **(06)**

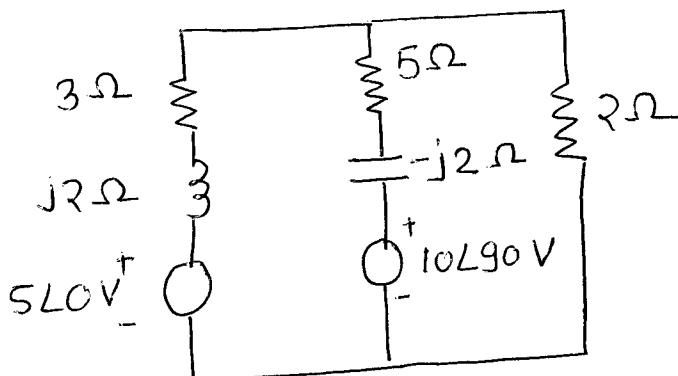b) Calculate current through 2Ω resistance by using Superposition theorem **(07)**




P.T.O.

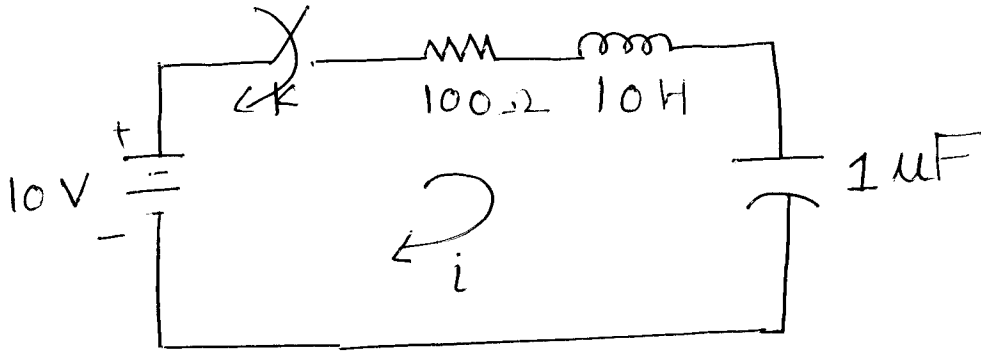- Q.3 a) In circuit Resistance R and inductance L is connected in series. With supply voltage V. Obtain expression for resulting Current $i(t)$ when switch is closed at $t = 0$. (06)
- b) In the circuit shown below, find $di(0^+)/dt$ of switch is closed at time $t = 0$ (07)



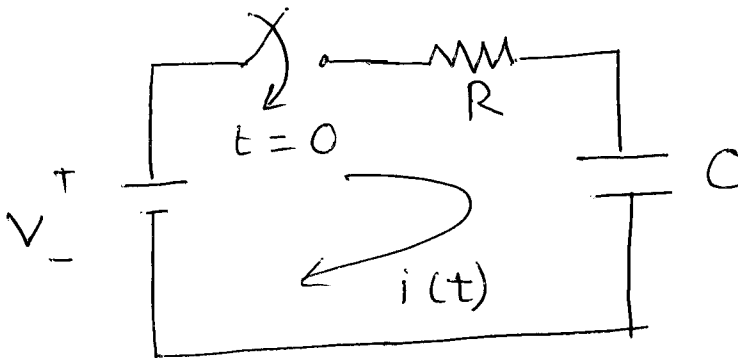
- Q.4 a) State and explain Laplace Transform of following function (06)
- Unit step function
 - Unit Ramp function
 - Unit impulse function
- b) For RC circuit shown in fig. Obtain expression for Current $i(t)$ at $t = 0$ (07)



SECTION - II

- Q.5 a) Express transmission parameters in terms of hybrid parameters. (05)
- b) What is the significance of poles and Zeros in concern with stability? (04)
- c) Define Even and odd symmetries of functions in Fourier analysis. (05)

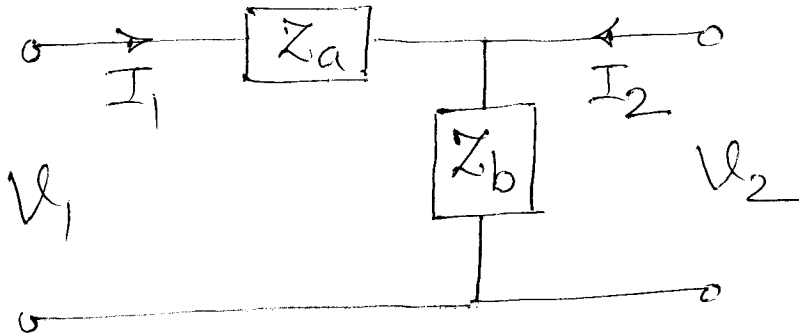
- Q.6 a) Find impedance parameters for the network shown. (07)



- b) Derive the condition of symmetry and Reciprocity in Transmission parameters. (06)


- Q.7 a) Define the following (06)
- Voltage ratio transfer function
 - Current ratio transfer function
 - Transfer Impedance
 - Transfer admittance

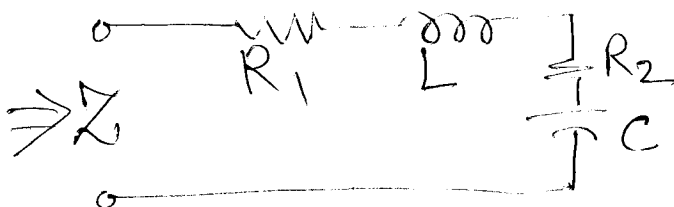- b) Find Driving point impedance of the network shown (07)



Q.8 a) Determine Fourier series for the waveform shown

(07)

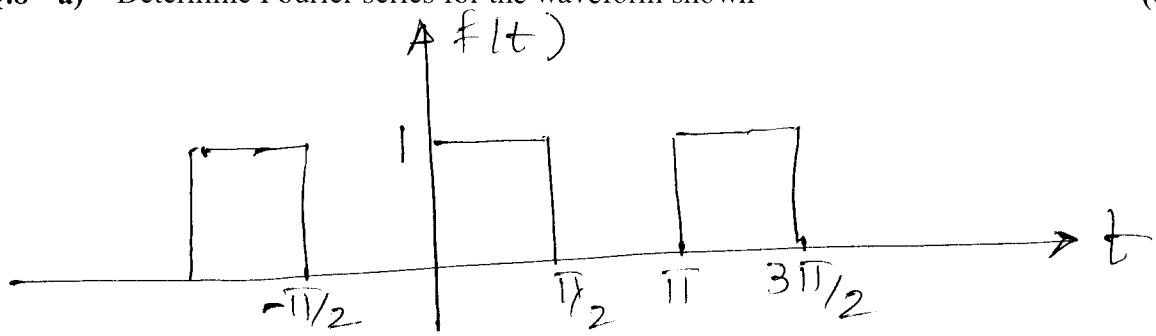

b) State & explain the trigonometric form of Fourier series.

(06)

* * *