

B. Tech. Sem -III (E & TC Engg.) (2014 COURSE) (CBCS) :

WINTER - 2018

SUBJECT : NETWORK THEORY

Day : Monday
Date : 03/12/2018


Time : 10.00 AM TO 01.00 PM
Max. Marks : 60

W-2018-2325


N. B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labeled diagram **WHEREVER** necessary.
- 4) Use of non-programmable calculator is **ALLOWED**.
- 5) Assume suitable data, if necessary.

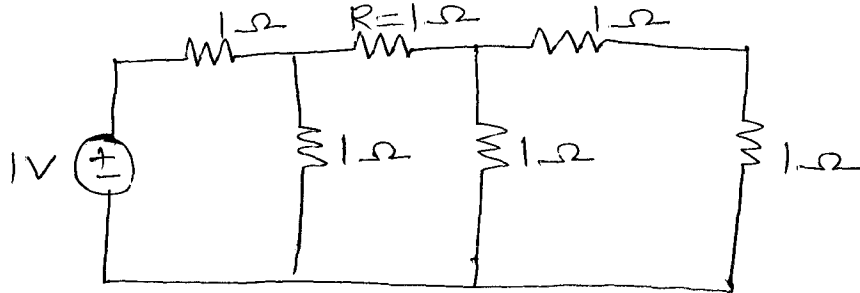Q. 1 a) Find the power dissipated in the resistor R in the ladder network shown: (05)




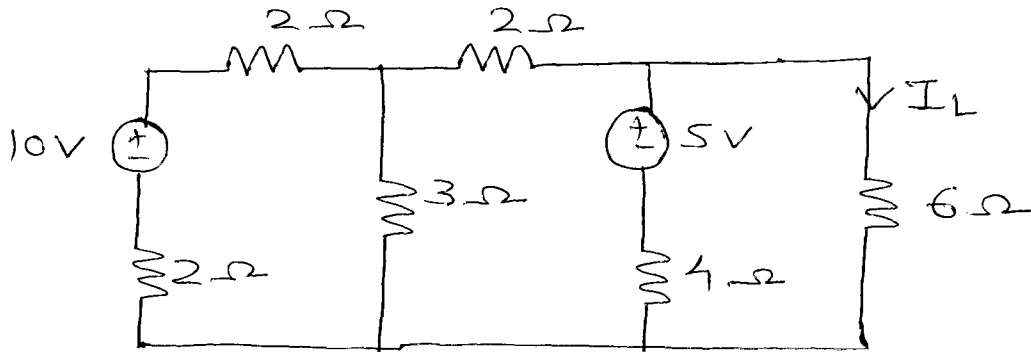b) Find the load current using superposition theorem. (05)




OR

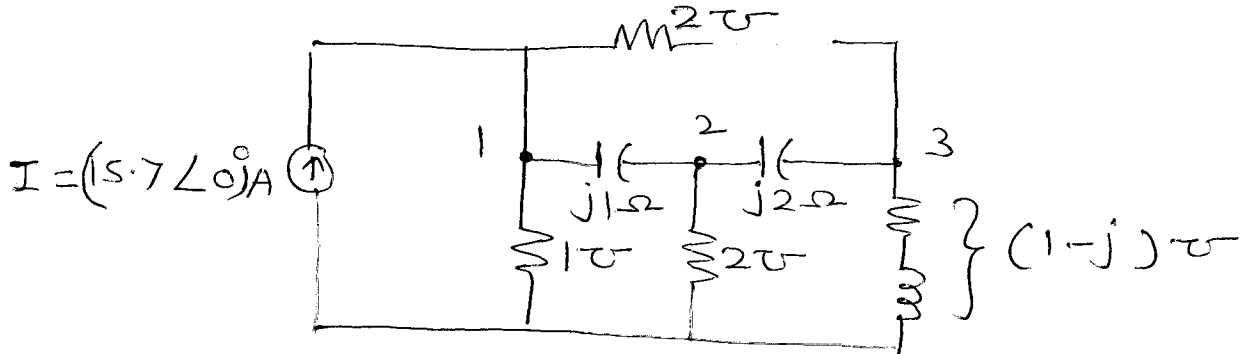a) Calculate the power delivered by the source in the shown circuit: (05)



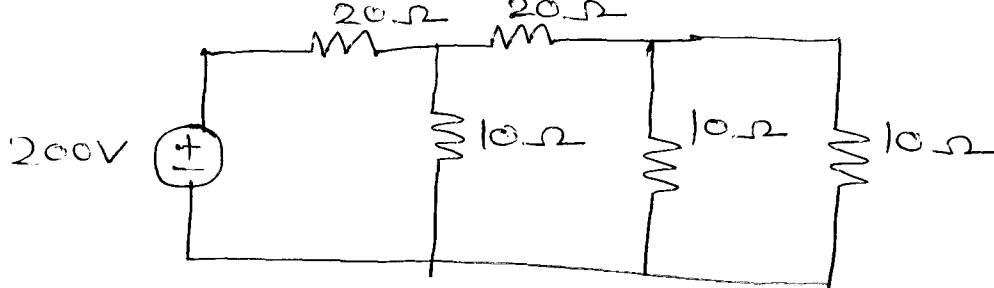b) For shown ladder network verify reciprocity theorem: (05)



P. T. O.


- Q. 2 a) Complete incidence matrix is given find total No. of trees for the concern matrix graph: (06)

$$Aa = \begin{bmatrix} -1 & 0 & 1 & 0 \\ 1 & -1 & 0 & -1 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$


- b) What is the condition of Isomorphpic graphs? (04)

OR

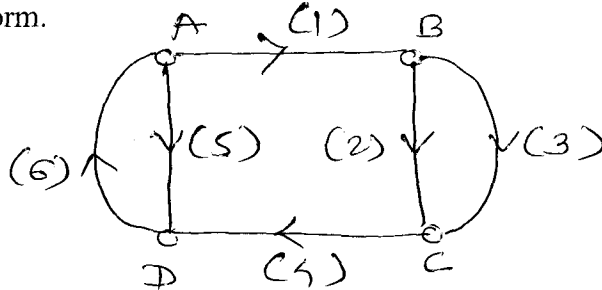- a) What is tieset? Find total No. of tiesets for the following graph and write it in matrix form. (05)



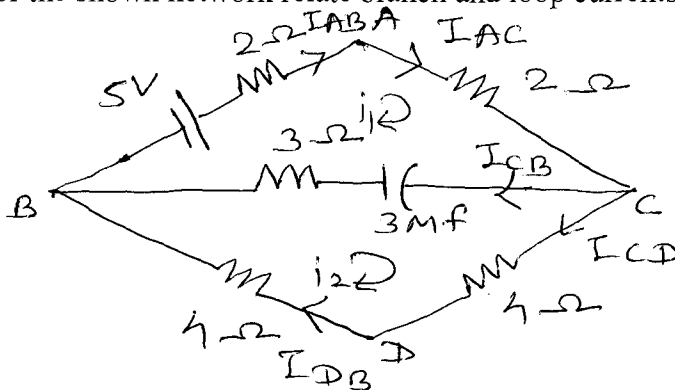- b) For the shown network relate branch and loop currents (05)




- Q. 3 a) Find transient response of driven RL circuit. (05)

- b) For series RC network switch will be closed at $t = 0$ with unchanged capacitor. (05)

Find: $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t = 0^+$. Given: $R = 2 k \Omega, V = 25v$ and $C = 2\mu f$.

OR

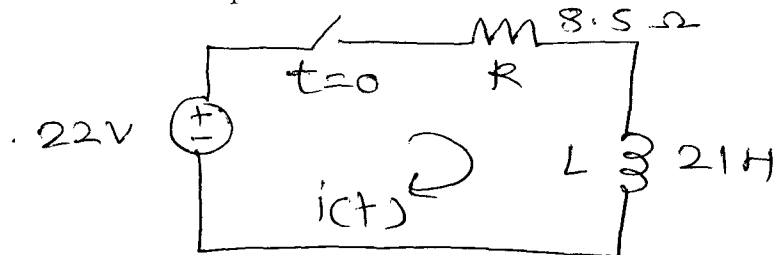- a) For the shown network, switch is kept open for long time. At $t = 0$, switch k is closed. Obtain expression for current in the circuit for $t > 0$. (05)



- b) Find transient response of undriven RC circuit. (05)

- Q. 4 a) Derive resonating frequency f_r for series RLC circuit. (04)

- b) A series circuit having capacitor of negligible resistance and coil of $120 \mu H$ with 18Ω resistance at 1 MHz. The circuit is driven by a generator at 1V, 1 MHz frequency with $R_g = 0 \Omega$. What will be the voltage across capacitor? What currents will flow at resonance? (06)

OR

- a) What is the difference between series and parallel resonant circuit? (05)
- b) A parallel circuit has a fixed capacitor and variable inductor having constant quality factor of 4, find value of inductance and capacitance for circuit impedance of $1\text{ k}\Omega$ at resonating frequency 2.4 MHz . (05)

- Q. 5**
- a) Design a constant k-LPF (T & π) with $F_c = 10\text{ KHz}$ and to work with characteristic resistance of $600\ \Omega$. (05)
 - b) Derive ZOT for m derived filter. (05)


OR

- a) Design m low pass T section having design impedance of $600\ \Omega$, a cut off frequency of 2 KHz and a frequency of infinite attenuation of 2100Hz . (05)
- b) What are the design formulae of k BPF? (05)

- Q. 6**
- a) Find symmetry and reciprocity conditions of ABCD parameters. (05)
 - b) When two networks are connected in series find Z parameter for the combined network? (05)

OR

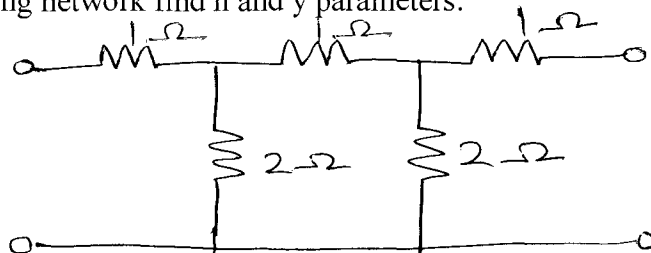- a) For the following network find h and y parameters: (05)



- b) Derive Y parameter in term of h parameter. (05)

* * * * *