

B.Tech Sem – V (2007 Course) (Electrical Engg.) : WINTER - 2018

SUBJECT: POWER ELECTRONICS

Day : Saturday
Date : 24/11/2018

Time : 02.30 PM TO 05.30 PM
Max. Marks : 80

W-2018-2803

N.B.:

- 1) **Q.No.1 and Q.No.5 are COMPULSORY.** Out of the remaining questions attempt **ANY TWO** questions from each section.
- 2) Answers to both the sections should be written in **SEPARATE** answer books.
- 3) Figures to the right indicate **FULL** marks.
- 4) Assume suitable data if necessary.

SECTION – I

- Q.1**
- a) Draw the Gate characteristics of SCR and explain it. (05)
 - b) Derive the expression for all external performance measures of 6 pulse converter. (04)
 - c) Explain the term breakdown voltage in DIAC. (04)
- Q.2**
- a) Draw the turn-off characteristics of SCR and explain the turn off mechanism. (07)
 - b) What are the different signals that can be used for turn on SCR by Gate control? Compare them. (06)
- Q.3**
- a) List the various techniques of improving power factor in phase controlled converter. (06)
 - b) Explain in detail the sinusoidal PWM control scheme for power factor improvement. (07)
- Q.4**
- a) Explain why the DIAC- TRIAC matched pair should be used in a control circuit. (07)
 - b) Draw and explain the VI characteristics of TRIAC and explain its working. (06)

SECTION – II

- Q.5**
- a) Draw and comment on VI characteristics of MCT. (05)
 - b) Draw the schematic diagram of a single phase AC chopper and discuss in brief the output voltage and current waveform. (04)
 - c) Explain in brief the difference between tripolar and unipolar PWM inverter. (04)
- Q.6**
- a) Explain the effect of temperature on the operation of MCT. (06)
 - b) With the help of neat sketch explain the operation of MOS- controlled thyristor (07)
- Q.7**
- a) Draw and explain the working of current commutated chopper. Also draw the associated waveform (07)
 - b) Describe the voltage commutated chopper with associated voltage and current waveform (06)
- Q.8**
- a) Explain the function of feedback diode used in anti parallel with transistor in inverter. (07)
 - b) Explain the cross-conduction of shoot through fault in inverter. How to overcome it? (06)

* * * *