

SUBJECT: RADIO FREQUENCY ENGINEERING

Day: Friday
Date: 30/11/2018

Time: 02.30 PM TO 05.30 PM
Max Marks. 60

W-2018-2599

N.B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Assume suitable data, if necessary.
- 4) Draw neat labeled diagrams **WHEREVER** necessary.

-
- | | | |
|------------|---|-------------|
| Q.1 | What is chip components? Explain chip and HF capacitors. | (10) |
| OR | | |
| Q.1 | Differentiate HF and chip resistors with neat diagram. | (10) |
| Q.2 | With neat diagram explain Vector Network analyzer? | (10) |
| OR | | |
| Q.2 | Explain with neat diagram short circuit time constant method. | (10) |
| Q.3 | Design common source amplifier with single tuned load. | (10) |
| OR | | |
| Q.3 | Describe different Bandwidth enhancement techniques. | (10) |
| Q.4 | Noise optimization with power. | (10) |
| OR | | |
| Q.4 | What are the noise parameters explain MOSFET. | (10) |
| Q.5 | What is RF oscillator explain with common gate FET. | (10) |
| OR | | |
| Q.5 | Describe function and startup module of colpitts oscillator. | (10) |
| Q.6 | Explain mixer fundamental with single ended diode mixer. | (10) |
| OR | | |
| Q.6 | What is RF mixer explain image reject mixer. | (10) |

* * * * *