

S.D.E.

B.C.A. (2004 Course Sem- II : WINTER - 2018

SUBJECT : DIGITAL COMPUTER DESIGN & COMPUTER ORGANISATION

Day : Wednesday
Date : 28/11/2018

W-2018-4506

Time : 10.00 AM TO 1.00 PM
Max. Marks : 80

N.B.

- 1) Attempt any **FIVE** questions from Section – I and any **TWO** questions from Section – II.
- 2) Figures to the right indicate **FULL** marks.
- 3) Answers to both the sections should be written in **SEPARATE** answer book.

SECTION – I

- Q.1** Explain different addressing modes with example. (10)
- Q.2** With neat circuit diagram explain 4:1 multiplexer. (10)
- Q.3** Differentiate between : (10)
a) Assembly Language and Machine Language
b) RISC and CISC
- Q.4** Explain action of shift register in detail. (10)
- Q.5** Describe Flip Flop in details: (10)
a) SR flip flop
b) JK flip flop
- Q.6** Explain the action of binary counter in detail. (10)
- Q.7** Write short notes on any **TWO**: (10)
a) Micro operation
b) Combinational circuit
c) Sequential circuit

SECTION – II

- Q.8** Plot the following Boolean equation function on:
k- map
 $F = \sum(0, 3, 4, 5, 6, 8, 10, 12)$ (15)
- Q.9** Define Interrupt. Discuss various types of Interrupts with their impact on instruction execution. (15)
- Q.10** Explain different types of logic gates with their Truth Table and symbol. (15)

* * *