

**F.Y.B.SC. (COMPUTER SCIENCE) SEM -II (2014 COURSE) :**  
**WINTER - 2017**  
**SUBJECT : LINEAR ELECTRONICS - II**

Day : Friday  
 Date : 03/11/2017

**W-2017-0740**

Time : 03.00 PM TO 05.00 PM  
 Max. Marks : 40

**N.B.:**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Use of Scientific calculator is **ALLOWED**.

**Q.1** Answer **ANY TWO** of the following: **[10]**


- a) Explain the working of on-line UPS with necessary block diagram.
- b) With neat diagram explain the working of Hartley oscillator. Also state the formula for its frequency.
- c) Explain the action of OP-AMP as adder with neat diagram.

**Q.2** Answer **ANY TWO** of the following: **[10]**

- a) Explain Wein bridge oscillator with necessary diagram. State equation for its output frequency.
- b) Define the following parameters for OP-AMP:
  - i) Slew rate
  - ii) Input bias current
  - iii) Output offset voltage
  - iv) Input impedance
  - v) CMRR
- c) Draw well labelled diagram for double ended input double ended output differential amplifier with constant current source. Explain it.

**Q.3** Answer **ANY TWO** of the following: **[10]**

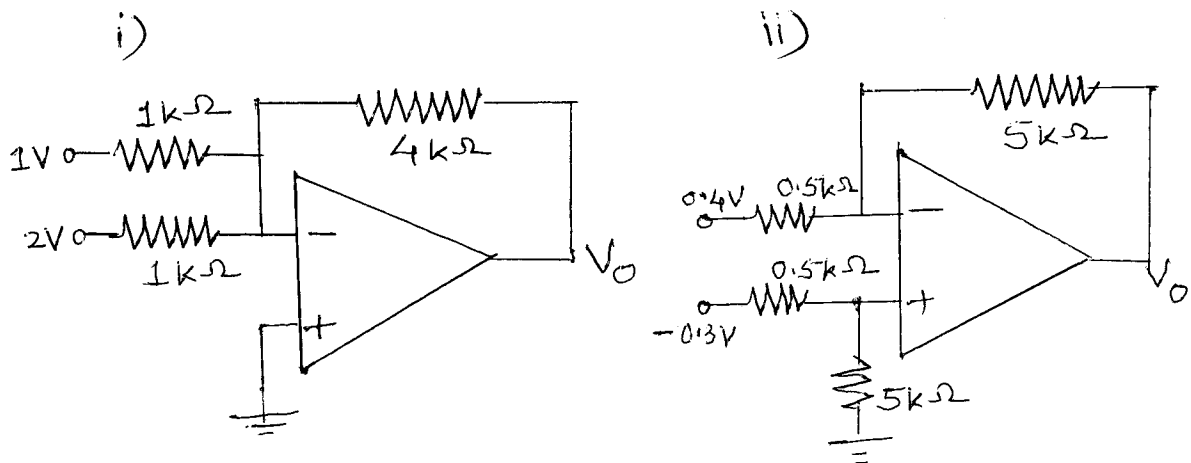- a) Draw block diagram for SMPS. Explain the function of each block.
- b) Explain the Barkhausen criteria for sustained oscillations.
- c) Identify the following circuits and find the output:



**Q.4** Answer **ANY FIVE** of the following: **[10]**

- a) Define the terms related to UPS:
  - i) Transition time
  - ii) Back up time.
- b) Draw the block diagram of regulated power supply.
- c) Explain the concept of virtual ground.
- d) State any four characteristics of an ideal OP-AMP.
- e) Find the frequency of oscillation for phase shift oscillator if  $R = 10k\Omega$  and  $C = 0.01\mu F$ .
- f) Define the following term for power supply:
  - i) Load regulation
  - ii) Line regulation
- g) State two points of difference between RC and LC oscillators.