

B. TECH. SEM -III (E & TC ENGG.) (2014 COURSE) (CBCS) :
WINTER - 2017
SUBJECT: DIGITAL CIRCUITS &APPLICATIONS

Day: **Friday**
Date: **19/01/2018**

Time: **10.00 AM TO 01.00 PM**
Max Marks. **60**

W-2017-2060

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Use of non – programmable calculator is **ALLOWED**.
- 4) Assume suitable data, if necessary.

Q.1 a) Minimize the following function using K – map and obtain the logic diagram **(05)**
from equation

$$f(A,B,C) = \Sigma m (1, 2, 3, 5, 7)$$

b) Convert Binary numbers 10110 and 1001011 to Grey code. **(05)**

OR

Q.1 a) State and prove Demorgan's Theorem. **(05)**

b) Simplify the expression and draw the logic diagram. **(05)**

$$Y = AB + A\bar{B}(\overline{AC})$$

Q.2 a) Explain full subtractor with truth table. **(05)**

b) What is Demultiplexer? Explain 4:1 Demux. **(05)**

OR

Q.2 a) What is priority encoder? **(05)**

b) What is ALU? **(05)**

Q.3 a) Explain CMOS NAND Gate. **(05)**

b) Differentiate TTL, ECL and CMOS. **(05)**

OR

Q.3 a) Define the following terms: **(05)**

- i) Power dissipation
- ii) Propagation delay
- iii) Noise margin
- iv) Operating temperature
- v) Fan – in

b) List out various logic families and explain any one in detail. **(05)**

P.T.O

Q.4 a) Explain operation of Master slave flip - flop and show how the race around condition is eliminated. **(05)**

b) Differentiate between Synchronous and Asynchronous circuit. **(05)**

OR

Q.4 a) What is JK flip – flop? Explain it with truth table. **(05)**

b) Differentiate between a Latch and a flip – flop. **(05)**

Q.5 a) Design MOD – 4 Asynchronous counter. **(05)**

b) Differentiate between Synchronous and Asynchronous counter. **(05)**

OR

Q.5 a) Define following terms: **(05)**

i) Setup time

ii) Hold time

iii) Rise time

iv) Fall time

b) What is Universal shift register? **(05)**

Q.6 a) Explain MOSFET RAM cell. **(05)**

b) What is PROM and explain types of PROM? **(05)**

OR

Q.6 a) What is meant by Static and Dynamic memory? **(05)**

b) Compare features of PROM, PAL and PLA. **(05)**

* * *
