

B.TECH SEM – IV (2007 COURSE) (ELECTRICAL ENGG.) :
WINTER - 2017
SUBJECT : LINEAR & DIGITAL INTEGRATED CIRCUITS

Day : **Monday** Time : **02.30 PM TO 05.30 PM**
Date : **20/11/2017** **W-2017-2410** Max. Marks : 80

N.B.:

- 1) **Q.No.1 and Q.No.5 are COMPULSORY.** Out of the remaining attempt **ANY TWO** questions from each section.
- 2) Answers to both the sections should be written in the **SEPARATE** answer books.
- 3) Use of non programmable **CALCULATOR** is allowed.
- 4) Figures to the right indicate **FULL** marks.
- 5) Assume suitable data if necessary.

SECTION – I

- Q.1** a) Define : i) Input offset voltage ii) Slew rate. [04]
b) Draw circuit diagram of precision half wave rectifier and explain the operation with waveforms. [05]
c) What are the applications of IC 556? Draw its block diagram. [05]
- Q.2** a) Draw pin diagram and equivalent circuit of operational amplifier. State open loop and closed loop gain of an amplifier and sketch its frequency response. [07]
b) Draw circuit of operational amplifier as non-inverting amplifier. With gain of 200 for input voltage of 10mv sinusoidal signal. Draw input and output waveforms. Describe virtual ground. [06]
- Q.3** a) Draw circuit diagram of inverting Schmitt trigger and describe its operation for sine wave input. State formula for UTP and LTP. [06]
b) Describe operation of precision full wave rectifiers with neat circuit diagram and waveforms. [07]
- Q.4** a) Draw block diagram of IC 8038. State its specifications and applications. [06]
b) Explain the operation of integrator using operational amplifier. [07]

SECTION – II

- Q.5** a) Perform the following using 2's complement method: [05]
i) $(64)_8 - (25)_8$ ii) $(69)_{10} - (32)_{10}$.
b) Explain IC 7485 (Digital Comparator). [05]
c) Write specification of CMOS family. [04]
- Q.6** a) Write a short note on ASCII code. [06]
b) Explain Hexadecimal number system. [07]
- Q.7** a) Describe characteristics of TTL family. [07]
b) Write a short note on tri state output. [06]
- Q.8** a) Write a short note on 4- bit ALU. [06]
b) Write the operation of Encoder with truth table. [07]

* * * *