

**B.TECH SEM - III (2007 COURSE) (ELECTRONICS) : WINTER -
2017**

SUBJECT : NETWORK ANALYSIS

Day : **Monday**
Date : **15/01/2018**

W-2017-2371


Time : **10.00 AM TO 01.00 PM**
Max. Marks : **80**

N.B.

- 1) Q.1 and Q.5 are **COMPULSORY**. Out of the remaining attempt any **TWO** questions from each section.
- 2) Figures to the right indicate **FULL** marks.
- 3) Answers to both the sections should be written in **SEPARATE** answer book.
- 4) Assume suitable data if necessary.
- 5) Use of non-programmable calculator is allowed.

SECTION - I

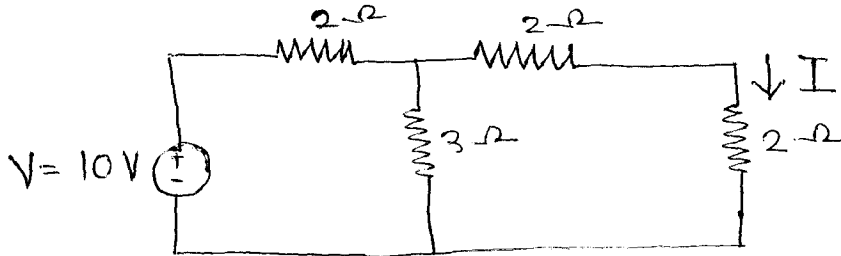- Q.1**
- a) Explain how source transformation is useful in the network analysis. **(05)**
 - b) What is the Q factor? Derive the expression for Q factor of capacitor. **(05)**
 - c) Explain electrical characteristics of asymmetrical network. **(04)**
- Q.2**
- a) State and explain : **(06)**
i) Superposition Theorem ii) Thevenin's Theorem
 - b) Verify the Reciprocity theorem for the voltage V and current I, in the network shown in the following figure: **(07)**



- Q.3**
- a) Derive expressions for voltages and currents for driven RL circuit. **(06)**
 - b) For the parallel resonant circuit, derive expression for : **(07)**
i) Resonant frequency ii) Q factor iii) Parallel resonant circuit as current amplifier.
- Q.4**
- a) Prove that in symmetrical T-network characteristic impedance is the geometric mean of the short circuit impedance and open circuit impedance. **(07)**
i.e. $Z_{OT} = \sqrt{Z_{oc} Z_{sc}}$.
 - b) A symmetrical T section composed of pure resistance has the values for open circuit and short circuit impedance $Z_{o/c} = 800 \angle 0^\circ \Omega$, $Z_{s/c} = 600 \Omega$ respectively. Determine Z_0 , Z_1 and Z_2 for T- network. **(06)**

P.T.O.

SECTION – II

- Q.5** a) Explain with reactance curves, constant K-type low pass filter. Also derive the expression for its cut-off frequency. **(05)**
- b) Explain in detail: **(04)**
i) Driving point impedance and admittance
ii) Transfer impedance and admittance.
- c) State the properties of RC driving point impedance functions. **(05)**
- Q.6** a) Design a T and π section high pass filter to work into impedance 500 Ω and have cut off frequency of 1 KHz. For this filter calculate phase angle ' β ' at frequency 1.5 KHz and attenuation ' α ' in neper at frequency of 0.9 KHz. **(07)**
- b) Compare prototype filter and m-derived filter. **(06)**
- Q.7** a) Derive the expressions for Y-parameters in terms of : **(07)**
i) Z-parameters ii) h-parameters
- b) Derive the conditions of symmetry for **(06)**
i) Y-parameters ii) ABCD parameters
- Q.8** a) Test whether $F(s) = \frac{S^2+1}{S^3+4S}$ is positive real function. **(06)**
- b) Check whether the following polynomials are Hurwitz. **(07)**
i) $F(S) = 2S^6 + S^5 + 13S^4 + 6S^3 + 56S^2 + 25S + 25$
ii) $F(S) = S^5 + 8S^4 + 24S^3 + 28S^2 + 23S + 6$

* * *