

**B. TECH. SEM -III (E & TC ENGG.) (2014 COURSE) (CBCS) :**  
**WINTER - 2017**  
**SUBJECT : NETWORK THEORY**

Day : Monday  
 Date : 22/01/2018

Time : 10.00 AM TO 01.00 PM  
 Max. Marks : 60


**W-2017-2061**

**N.B.:**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Use of non-programmable **CALCULATOR** is allowed.
- 4) Draw neat and labeled diagram **WHEREVER** necessary.
- 5) Assume suitable data if necessary.


**Q.1 a)** Two storage batteries A and B are connected in parallel for charging from a d.c. source having an open circuit voltage of 14V and internal resistance of  $0.15\Omega$ . The open circuit voltage of A is 11V and that of B is 11.5V. Their internal resistances are  $0.06\Omega$  and  $0.05\Omega$  respectively. Calculate the initial charging currents and the source current. **[06]**

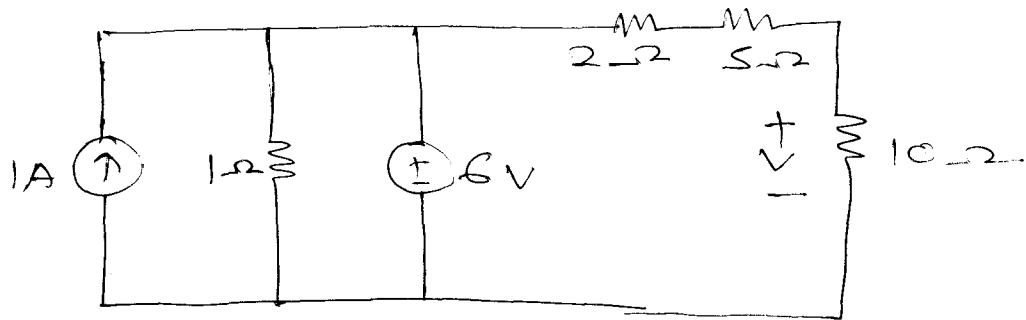**b)** Using source transformation find the voltage V for the shown circuit. **[04]**




**OR**

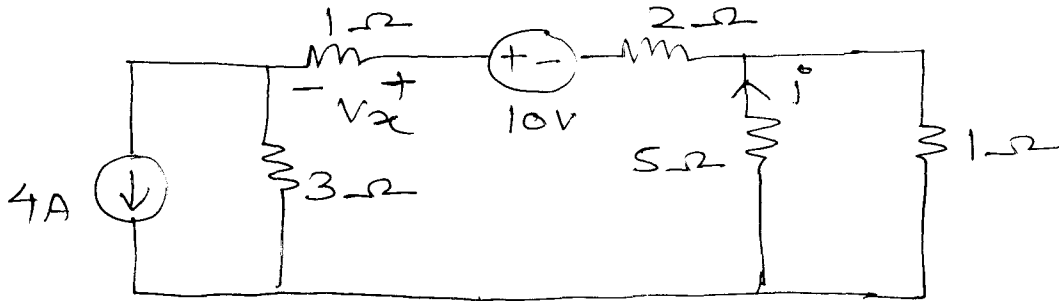**a)** Find current (i) and voltage ( $V_x$ ) in the figure given below. **[06]**




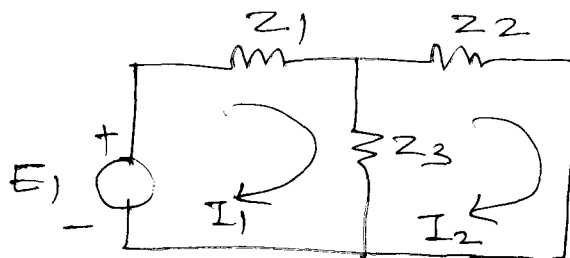**b)** What will be the condition of reciprocating for following circuit? **[04]**




**P.T.O.**

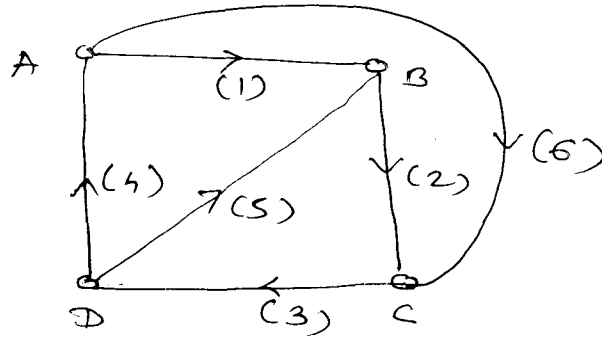Q.2 a) Find out cut sets for the given graph. [05]



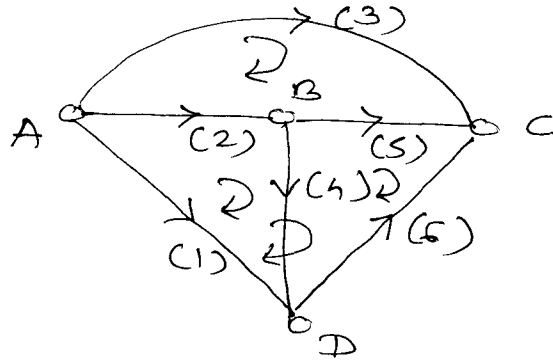b) Define f-circuits. What will be the rank of f-circuits? [05]



OR

a) Compare incidence matrix and cut-set matrix. [05]

b) Draw the oriented graph from reduced incidence matrix and find number of trees for the graph. [05]


$$A = \begin{bmatrix} -1 & 0 & 1 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 \end{bmatrix}$$

Q.3 a) For the shown network switch K will be closed at  $t = 0$  with capacitor uncharged. Find the value of  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ . Given that  $V = 120V$ ,  $R = 2k\Omega$  and  $C = 0.1\mu F$ . [07]

b) What is the procedure for evaluating initial conditions? [03]

OR

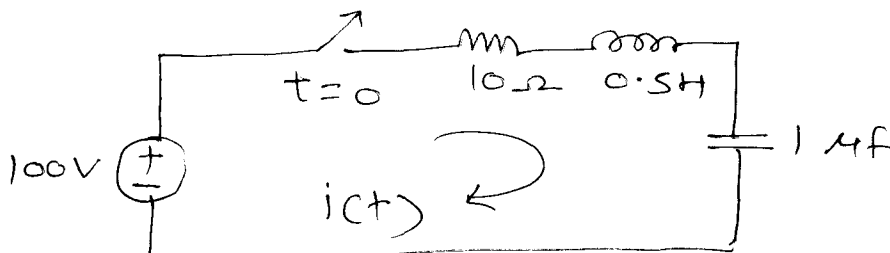a) Obtain current  $i(t)$  for  $t \geq 0$  using time approach. [07]



b) What is the need of initial condition? [03]

- Q.4** a) Derive quality factor of series RLC circuit. [05]
- b) An RLC series circuit has  $R = 1\text{K}\Omega$ ,  $L = 100\text{mH}$ ,  $C = 10\mu\text{F}$ . If a voltage of 100 is applied across the series combination, determine: [05]
- Resonant – frequency
  - Q factor
  - Half power frequencies

**OR**

- a) Derive anti-resonance frequency. [07]
- b) A series RLC circuit has  $R = 30\Omega$ ,  $L = 0.06\text{H}$  and  $C = 0.02\mu\text{F}$ . Calculate series resonance frequency. [05]

- Q.5** a) A prototype LPF is to be designed which must have  $R_0 = 600\Omega$  and  $f_c = 1\text{KHz}$ . Find the filter elements. [05]
- b) What is composite filter? [05]

**OR**


- a) What are the disadvantages of prototype filters? [04]
- b) Find  $m$  – derived T and  $\pi$  sections having a cut-off frequency of  $f_c = 1\text{KHz}$  and a design impedance ( $R_0$ ) =  $600\Omega$ . The filter must have infinite attenuation  $f_\infty = 1050\text{ Hz}$ . [06]

- Q.6** a) Determine the h parameters with the following data: [05]
- with output shorted  
 $V_1 = 30\text{V}$ ,  $I_1 = 1.5\text{A}$ ,  $I_2 = 1.5\text{A}$ .
  - with input terminals open circuited  
 $V_1 = 15\text{V}$ ,  $V_2 = 75\text{V}$ ,  $I_2 = 2\text{A}$

- b) Derive transmission parameters in terms of z parameters. [05]

**OR**

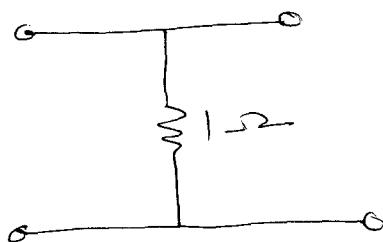- a) Determine z, h and y parameter of the shown network. [05]



- b) Show that the h parameters will not exist for a two port network when  $z_{22} = 0$ . [05]

\* \* \* \*