

B.TECH SEM - III (2007 COURSE) (BIOMEDICAL ENGG.) :
WINTER - 2017
SUBJECT : NETWORK THEORY

Day : Monday
Date : 22/01/2018

W-2017-2390


Time : 10.00 AM TO 01.00 PM
Max. Marks : 80

N.B.

- 1) Q.1 and Q.5 are **COMPULSORY**. Out of the remaining attempt any **TWO** questions from each section.
- 2) Figures to the right indicate **FULL** marks.
- 3) Answers to both the sections should be written in **SEPARATE** answer book.
- 4) Assume suitable data if necessary.
- 5) Use of non-programmable calculator is allowed.

SECTION - I

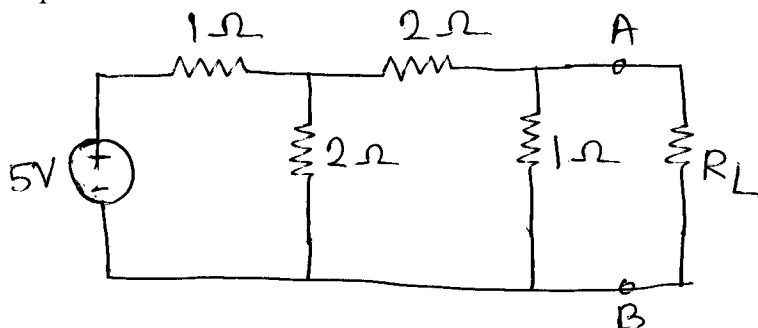- Q.1**
- a) Explain how source transformation is useful in circuit analysis. **(04)**
 - b) What is the Q factor? Derive the expression for Q factor of capacitor. **(05)**
 - c) For an asymmetrical four terminal network, explain the terms:
i) Image impedance ii) Iterative impedance. **(05)**
- Q.2**
- a) State and prove superposition theorem. **(06)**
 - b) For the circuit shown in following figure, find value of resistance R_L , that will determine the maximum power transfer. Also find value of maximum power delivered to R_L **(07)**



- Q.3**
- a) Explain initial conditions in various elements. **(06)**
 - b) Find the values of R, L and C in a series RLC circuit that resonates at 1.5KHz and consume 50W from a 50V ac source operating at the resonant frequency. The bandwidth is 0.75 KHZ. **(07)**
- Q.4**
- a) Explain the electrical properties of symmetrical two port network. **(05)**
 - b) Derive the expressions for the characteristic impedance of symmetrical T and π network and hence show that $Z_{OT}Z_{O\pi} = Z_1Z_2$. **(08)**

P.T.O.

SECTION – II

- Q.5** a) Draw a circuit of a band stop filter. Sketch the reactance curves for the same showing pass and stop bands. **(04)**
- b) What is the significance of poles and zeros in s-plane? **(05)**
- c) State the properties of Hurwitz polynomials. **(05)**
- Q.6** a) What are the disadvantages of prototype filter? How are they corrected in the m-derived filter? Draw the block schematic of composite filter. **(06)**
- b) Design a prototype low pass filter having cut-off frequency of 1KHz and design impedance of 400Ω. **(07)**
- Q.7** a) Derive the expressions for Y-parameters in terms of Z-parameters and H-parameters. **(07)**
- b) Derive the conditions of symmetry and reciprocity for:
i) ABCD parameters ii) H-parameters. **(06)**
- Q.8** a) Find the Forster – I form of the RL impedance function **(06)**
$$Z(S) = \frac{(S+1)(S+4)}{(S+5)(S+3)}$$
- b) Test whether the following polynomials are Hurwitz. **(07)**
i) $P(S) = 2S^6 + S^5 + 13S^4 + 6S^3 + 56S^2 + 25S + 25$
ii) $P(S) = S^5 + 8S^4 + 24S^3 + 28S^2 + 23S + 6$

* * *