

B.TECH. SEM -VI ELECTRICAL 2014 COURSE (CBCS) :

WINTER - 2017

SUBJECT : POWER SYSTEM ANALYSIS

Day : **Tuesday**
Date : **21/11/2017**

W-2017-2202

Time : **10.00 AM TO 01.00 PM**
Max. Marks : 60

N.B.:

- 1) All questions are **COMPULSORY**.
 - 2) Figures to the right indicate **FULL** marks.
 - 3) Assume suitable data if necessary.
-

Q.1 Derive expression for complex power flow over a transmission line and justify P-f and Q-V dependency. [10]

OR

- a) Two voltage sources $V_1 = 110 \angle -5^\circ$ V and $V_2 = 100 \angle -0^\circ$ V are connected by a transmission line whose impedance is $(1 + j7) \Omega$. Determine the real and reactive power supplied by or received by each source. [05]
- b) Derive the equation of real and reactive power. Comment on the parameters that can control real and reactive power flows. [05]

Q.2 Derive equivalent π circuit of a long transmission line. Derive constants of this circuit in hyperbolic form. [10]

OR

- a) State the assumptions used to convert the impedance diagram to reactance diagram of a power system. [05]
- b) A 5 KVA, 400/200V, 50Hz, single-phase transformer has primary and secondary leakage reactance each of 2.5Ω . Determine the total reactance in per unit. [05]

Q.3 a) Write short note on formation of power-flow equations. [05]

- b) Classify different types of buses in power system for load flow studies and explain their significance in brief. [05]

OR

Explain Newton-Raphson method used to solve the load-flow equations with flow chart. [10]

Q.4 a) What is the requirement of selection of circuit breakers? [05]

- b) Find the value in ohms of the reactance per phase external to a 20 MVA, 10KV, 50 Hz, 3-phase generator such that the steady-state current on short-circuit shall not exceed 8 times the full-load current. The internal reactance of the generator is 5%. [05]

P.T.O.

OR

Derive an expression for short circuit current of an unloaded 3 ϕ alternator. [10]
Sketch : i) DC off-set component ii) Symmetrical short circuit component.

- Q.5** a) Sketch the sequence networks of a 3 ϕ synchronous alternator. [05]
- b) For a Line-to-Ground (L-G) fault draw the sequence diagram and derive relationship between symmetrical component currents and phase currents. [05]

OR

- a) List out the different kinds of symmetrical and unsymmetrical faults. [04]
- b) A 20MVA, 33KV, 3 ϕ alternator is subjected to different types of short-circuits and the following are the values of the fault currents: [06]
- | | |
|------------------------|---------|
| 3-phase short circuit | = 319 A |
| Line – to ground fault | = 659 A |
| Line – to – line fault | = 435A |
- Assuming a generator e.m.f. of 1 per unit and no-load condition before the occurrences of the faults. Determine the positive, negative and zero-sequence reactances of the generator in per unit.

- Q.6** a) Derive swing equation of one machine infinite bus system. [06]
- b) Define steady state stability and transient stability of power system. [04]

OR

Discuss transient stability of one machine infinite bus power system with reference to the following points: [10]
Definition, dynamics of synchronous machine, swing equation and its significance.

* * * *