

S.D.E.

B.C.A. (2004 COURSE SEM- II : WINTER - 2017

SUBJECT : DIGITAL COMPUTER DESIGN AND COMPUTER ORGANIZATION

Day : Tuesday  
Date : 12/12/2017

W-2017-4153

Time : 02.00 PM TO 05.00 PM  
Max. Marks : 80

N. B. :

- 1) Attempt **ANY FIVE** questions from Section – I and attempt **ANY TWO** questions from Section – II.
- 2) Figures to the right indicate **FULL** marks.
- 3) Answers to both the sections should be written in the **SEPARATE** answer books.
- 4) Draw neat diagram **WHEREVER** necessary.

SECTION – I

- Q. 1 Differentiate between: (10)
- a) Digital computers and Analog computers
  - b) Hardwired control unit and Micro-programmed control unit
- Q. 2 Discuss the full adder with help of circuit diagram and truth table. (10)
- Q. 3 What is decoder? Explain the functioning of 3 to 8 line decoder. (10)
- Q. 4 Why register transfer is essential? Explain register transfer with help of register transfer language. (10)
- Q. 5 Give basic computer instruction formats with examples. (10)
- Q. 6 Explain the terms: (10)
- a) Assembler
  - b) Program interrupt
  - c) Subroutines
- Q7 Write short notes on **ANY TWO** of the following: (10)
- a) Program loop
  - b) Design of basic computer
  - c) Memory unit

SECTION - II

- Q. 8 a) Simplify using Boolean algebra: (08)
- i)  $(BC' + A'D)(AB' + CD')$
  - ii)  $A'B + ABC' + ABC$
- b) Simplify using K map. (07)  
 $F(A,B,C)=\sum(0,2,3,4,6)$
- Q. 9 Explain the working of 4 bit binary counter using circuit diagram. (15)
- Q. 10 Draw the block diagram of 4 bit arithmetic circuit and explain it with function table. (15)

\* \* \* \* \*