

**CDOE**  
**BACHELOR OF COMPUTER APPLICATIONS (CBCS-2019 COURSE)**  
**B.C.A. SEM - II : WINTER :- 2021**  
**SUBJECT: COMPUTER ORGANIZATION & ARCHITECTURE**

**Day : Monday**  
**Date 7/2/2022**

**W-21857-2021**

**Time : 10:00 AM-01:00 PM**  
**Max. Marks: 60**

**N.B.:**

- 1) Q 4 from Section-I is COMPULSORY.
- 2) Answer ANY TWO questions from Q 1, 2, 3 in Section-I.
- 3) Answer ANY TWO questions from Q 5, 6, 7 in Section-II.
- 4) All question CARRY EQUAL marks.
- 5) Answers to Both the sections to be written in SAME answer book.
- 6) Draw a labeled diagram WHEREVER necessary.

**SECTION - I**

Q.1) Answer the following: (6 Marks X 2 = 12)

- a) Explain working of 4 bit adder-subtractor with help of diagram.
- b) Draw the circuit of 4 bit synchronous binary counter and give its functioning.

Q.2) Answer the following: (6 Marks X 2 = 12)

- a) What is instruction cycle? Explain instruction cycle with help of flowchart.
- b) Discuss the different mapping techniques used in cache memories with their relative merits and demerits.

Q.3) Explain the following: (6 Marks X 2 = 12)

- a) What is an addressing mode? Describe various addressing modes that exist in a modern processor.
- b) Explain asynchronous data transfer with strobe control and handshaking method.

Q.4) Write short notes on the following: Attempt ANY THREE (4 Marks X 3 = 12)

- a) Assembler
- b) Need of interface
- c) RISC
- d) Instruction formats
- e) Multiplexer

**SECTION - II**

Q.5) Answer the following: (12 Marks X 1 = 12)

The sequential circuit has two D flip flops A and B, two inputs x and y, and one output z. The flip-flop input equations and circuit output is as follows.

$$D_A = x'A + y'B'$$

$$D_B = y'B + xA$$

$$z = xy + x'B$$

- i) Draw logic diagram.
- ii) Tabulate state table.

Q.6) Answer the following: (6 Marks X 2 = 12)

- a) Draw the circuit diagram and tabulate the truth table.

$$(A + C)(AD + AD') + AC + C$$

- b) Solve the following.

- i. Find 2's complement of: 01111100
- ii. 10000010 - 01010101 using 2's complement method.
- iii. 110 \* 110

Q.7) Explain the following: (12 Marks X 1 = 12)

Draw the block diagram of 4 bit arithmetic circuit and explain the functioning of it.

\*\*\*\*\*