

BACHELOR OF SCIENCE (COMPUTER SCIENCE) (CBCS - 2018 COURSE)
F.Y.B.Sc.(Computer Science) Sem-I :SUMMER- 2022
SUBJECT : PRINCIPLES OF ANALOG ELECTRONICS-I

Day : Tuesday
Date : 12/7/2022

S-20070-2022

Time : 11:00 AM-02:00 PM
Max. Marks : 60

N.B.


- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw diagrams **WHEREVER** necessary.
- 4) Use of calculator is **ALLOWED**.

Q.1 Attempt any **TWO** of the following: **(12)**

- a) i) With neat diagram explain the action of transistor as a switch.
ii) Define α and β for transistor.
- b) Explain the working principle of n – channel FET.
- c) Explain the action of Light Dependent Resistor. Also draw symbol for it.

Q.2 Attempt any **TWO** of the following: **(12)**

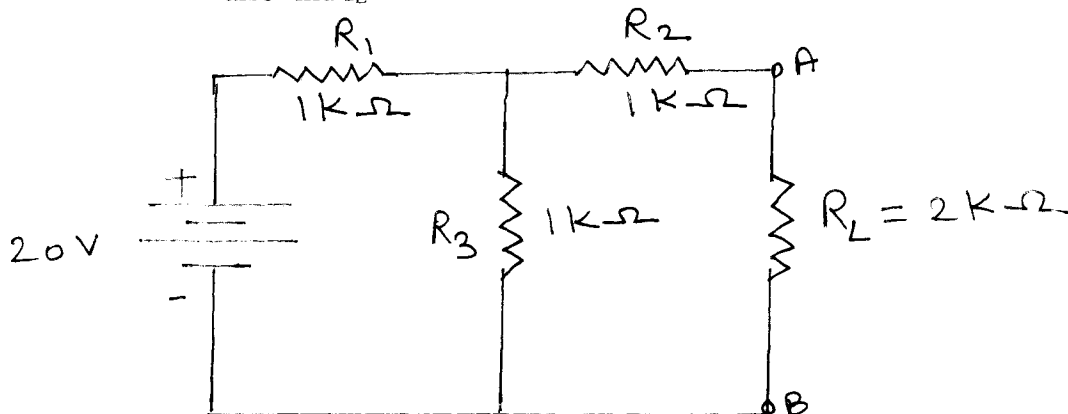- a) i) Explain the working of NPN transistor with neat diagram.
ii) State different configurations of transistor .
- b) With neat diagram explain the working of N – channel enhancement MOSFET.
- c) i) Give the statement for Thevenin's theorem.
ii) Determine Thevenin's equivalent circuit for the following network and also find I_L



Q.3 Attempt any **TWO** of the following: **(12)**

- a) With neat diagram explain the working principle of UJT. Also define intrinsic stand – off ratio for it.
- b) Obtain expressions for growth and decay of current for RC circuit.
- c) Draw and explain the output characteristics for transistor in CE – mode.


P.T.O.

Q.4

Attempt any **THREE** of the following:

(12)

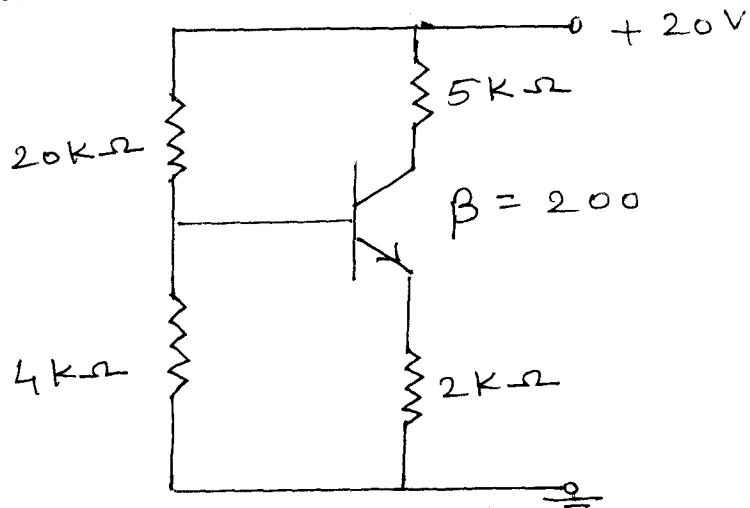- a) Draw dc load line for the following circuit and locate Q – point. Assume the transistor to be of silicon.



- b) Explain the classification of amplifiers on the basis of frequency response.
- c) Explain the working principle of transformer. Give different types of transformers.
- d) Give the statements for the following:
- Maximum power transfer theorem
 - Nortan's theorem

Q.5

Attempt any **FOUR** of the following:

(12)

- a) Define the following terms for resistor
- Tolerance
 - Power rating
 - Temperature coefficient
- b) For a bipolar junction transistor if base current is 35 μA and collector current is 10 mA, find α , β and current flowing through the emitter of the transistor.
- c) Define the following parameters of JFET:
- Drain resistance
 - Transconductance
 - Amplification factor
- d) Draw equivalent circuit for SCR and also its symbol.
- e) Draw well – labelled diagram for RC coupled CE amplifier.
- f) State three points of difference between JFET and MOSFET.

*

*

*