

BACHELOR OF SCIENCE (COMPUTER SCIENCE) (CBCS - 2018 COURSE)
S.Y.B.Sc.(Computer Science) Sem-IV :SUMMER- 2022
SUBJECT : ANALOG SYSTEMS

Day : Wednesday
Date : 13-07-2022

S-20108-2022

Time : 03:00 PM-06:00 PM
Max. Marks : 60

N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate full marks.
- 3) Draw diagrams **WHEREVER** necessary.
- 4) Use of Calculator is **ALLOWED**.

Q.1 Answer **ANY TWO** of the following: (12)

- a) Explain the working of water level indicator system using float switch.
- b) Explain with diagram the working of a balanced Wheatstone's bridge.
- c) With neat diagram explain the construction and working principle of LVDT.

Q.2 Answer **ANY TWO** of the following: (12)

- a) Explain the operating principle of capacitive touch sensors. State any two applications of it.
- b) Draw well-labelled diagram of three OP-AMP instrumentation amplifier. Derive the equations for its gain.
- c) Draw simplified block diagram of ECG system and explain analysis of ECG signal.

Q.3 Answer **ANY TWO** of the following: (12)

- a) State and explain any six specifications of sensors.
- b) Explain first order low pass filter with its frequency response. State any two applications of it.
- c) Explain the working of temperature monitoring system using LM-35.

Q.4 Answer **ANY THREE** of the following: (12)

- a) State the basic principle of working of ultrasonic sensor. State any two applications of it.
- b) State four points of difference between active and passive filters.
- c) Explain the working principle of pH sensor.
- d) Draw block diagram of an analog electronic system and state the role of sensors.

Q.5 Answer **ANY FOUR** of the following: (12)

- a) Calculate the current through galvanometer of an unbalanced Wheatstone's bridge with excitation voltage of 12V and $R_1 = 1k\Omega$, $R_2 = 4K\Omega$, $R_3 = 3K\Omega$, $R_4 = 8K\Omega$ and $R_g = 600\Omega$.
- b) Define the following terms:
i) Sensors ii) Transducers iii) Instrumentation
- c) Explain switch based tilt sensors.
- d) Draw frequency response for band pass filter.
- e) List any three features of AD590.
- f) List any three application of PIR sensors.

* * * * *