

**BACHELOR OF COMPUTER APPLICATIONS (CBCS - 2018 COURSE)**

**B.C.A. Sem-II :SUMMER- 2022**

**SUBJECT : COMPUTER ORGANIZATION & ARCHITECTURE**

Day : Monday

Date : 6/6/2022

**S-18759-2022**

Time : 10:00 AM-01:00 PM

Max. Marks : 60

**N.B.:**

- 1) **Q. No. 4** from Section –I is **COMPULSORY**.
- 2) Answer any **TWO** questions from Questions **1, 2 & 3** in **Section –I**.
- 3) Answer any **TWO** questions from Questions **5, 6 & 7** in **Section –II**.
- 4) Figures to the right indicate **FULL** marks.
- 5) Answers to both the sections should be written in **SAME** answer book.

**SECTION-I**

- Q.1** a) What are different types of addressing modes? Explain six addressing modes with proper example. (06)  
b) With the help of proper diagram, discuss Memory Hierarchy. (06)
- Q.2** a) Construct and discuss 3 x 8 decoder with the help of 2x4 decoder. (06)  
b) Explain various instruction formats with the help of examples. (06)
- Q.3** a) Discuss term Machine Language, Assembly Language and Assembler. (06)  
b) Explain instruction cycle with the help of flow chart. (06)
- Q.4** Write short notes on any **THREE** of the following: (12)  
a) Flip Flop  
b) Bus and Memory Transfer  
c) Peripheral Devices  
d) Types of interrupts  
e) Number system

**SECTION-II**

- Q.5** a) Draw the circuit diagram and tabulate the truth table. (06)  
 $(BC' + A'D)(AB + CD')$   
b) Prove  $A + A'B + A'B'C + A'B'C'D = A + B + C + D$  (06)
- Q.6** Solve the following: (12)  
a) Simplify the following Boolean function using K-map  
 $F(A, B, C, D) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$   
b)  $10010 * 111$   
c)  $10000010 - 01010101$  using 2's complement method.
- Q.7** A sequential circuit with two D flip-flops A and B, two inputs x and y and one output z is specified by the following input equations: (12)  
 $D_A = x'y + xA$   
 $D_B = x'B + yA'$   
 $Z = xA + yB'$   
a) Draw logic diagram  
b) Derive the state diagram  
c) Derive the state table

\* \* \* \*