

**BACHELOR OF TECHNOLOGY (C.B.C.S.) (2014 COURSE)**

**B.Tech.Sem - V E & TC : : SUMMER - 2022**

**SUBJECT : POWER DEVICES & MACHINES**

Day : Thursday  
Date : 2/6/2022

**S-13359-2022**

Time : 10:00 AM-01:00 PM  
Max. Marks : 60

---

**N.B.**

- 1) All questions are **COMPULSORY**.
  - 2) Figures to the right indicate **FULL** marks.
  - 3) Use of Non-programmable **CALCULATOR** is allowed.
  - 4) Assume suitable data if necessary.
- 

**Q.1** Explain power diodes with respect to its construction, switching characteristics and line frequency. (10)

**OR**

With the help of circuit diagram explain Gate drive circuit for MOSFET and IGBT. (10)

**Q.2** Explain triggering and isolation techniques of SCR, also explain two transistor analogy of SCR. (10)

**OR**

Explain GTO with respect to construction, operational characteristics and applications. (10)

**Q.3** For higher power application why three phase system is preferred over a single phase? Also explain the effect of freewheeling diode. (10)

**OR**

With the help of circuit diagram and operational waveform explain single phase full converter for RL load. (10)

**Q.4** Describe DC chopper with all its control strategies and operational results. (10)

**OR**

Explain single phase bridge inverter for RL load with its working principle and operational results. (10)

**Q.5** Write a note on DC Motor in detail with its construction, working principles and applications. (10)

**OR**

Explain Induction Motor with respect to construction, working principles and applications. (10)

**Q.6** Describe ON line UPS and OFF line UPS in detail. (10)

**OR**

Write different speed control techniques in industrial applications. (10)

\* \* \* \*