

**BACHELOR OF TECHNOLOGY (C.B.C.S.) (2014 COURSE)**  
**B.Tech.Sem - VI ELECTRONIC :SUMMER- 2022**  
**SUBJECT : VLSI DESIGN**

Day : Friday  
Date : 17-06-2022

**S-13390-2022**

Time : 02:30 PM-05:30 PM  
Max. Marks : 60

---

**N.B.:**

- 1) All questions are **COMPULSORY**.
  - 2) Figures to the right indicate **FULL** marks.
  - 3) Use of non-programmable **CALCULATOR** is allowed.
  - 4) Draw neat and labeled diagrams **WHEREVER** is allowed.
  - 5) Assume suitable data if necessary.
- 

**Q.1** What is the need of attributes in VHDL? Explain any three attributes with suitable example. (10)

**OR**

Write VHDL code for 4-bit binary up/down counter. (10)

**Q.2** What do you mean by measurability? What are the solutions? Explain any one in detail. (10)

**OR**

Design 110... sequence detector using VHDL with Moore Machine. (10)

**Q.3** Draw the architecture of FPGA XC4000. Explore logic cell and interconnect matrix. (10)

**OR**

What is the function of 'bus hold logic' and 'hot plugging capability' in CPLD? Describe TAP controller. (10)

**Q.4** Define MOSFET and describe the fabrication procedure. (10)

**OR**

Discuss the MOSFET current -voltage characteristics. (10)

**Q.5** Define stick diagram and layout diagram. Design the stick diagram of CMOS inverter. (10)

**OR**

Describe static power and dynamic power dissipation. (10)

**Q.6** Design two-input NAND gate using CMOS. (10)

**OR**

Design the CMOS logic circuit for the given expression. (10)

$$y = \overline{A + B + C}$$

\* \* \* \* \*