

BACHELOR OF TECHNOLOGY (C.B.C.S.) (2020 COURSE)
B.Tech.Sem - IV R&A :SUMMER- 2022
SUBJECT : POWER ELECTRONICS & DRIVES

Day : Monday
Date : 20-06-2022

S-24788-2022

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labelled diagram **WHEREVER** necessary.
- 4) Assume suitable data, if necessary.

-
- Q.1** a) Explain any one voltage control techniques in voltage source inverter with require D circuit diagram. (05)
b) Compare the different types of pulse width modulation technique. (05)
- OR**
- Q.1** Explain the working of three phase 180° mode of voltage source inverter with circuit diagram and switching table. Draw line and phase voltage waveform for any one phase. (10)
- Q.2** a) Explain the operation of line commutated current source inverter with waveform. (05)
b) Write the comparison between voltage and current source inverter. (05)
- OR**
- Q.2** What is matrix converter? Draw the circuit diagram of 3 x 3 matrix converter and write the voltage, current equation matrix. (10)
- Q.3** a) What are the different applications of multilevel inverter, explain any one application with required diagram. (05)
b) Draw the switching table of diode clamped multilevel inverter and explain its operation. (05)
- OR**
- Q.3** What is the basic concept of mutilevel inverter? Write its basic features, equation and draw general topology diagram with waveform. (10)
- Q.4** a) Explain with the neat diagram and waveform operation of single phase full converter drive fed separately excited DC motor. (05)
b) What is DC servo drive? Explain in brief. (05)
- OR**
- Q.4** A 220 V, 1500 RPM, 10 A, separately excited dc motor has an armature resistance of 1Ω . It is fed from a single phase fully controlled bridge rectifier with an ac source voltage of 230 V, 50 Hz. Compute:
i) motor speed at firing angle of 30° and torque of 5 N-m. (10)
ii) Developed torque at firing angle of 45° and speed of 1000 rpm.
- Q.5** a) Explain with the circuit diagram stator voltage control technique for 3 phase induction motor. (05)
b) With the help of block diagram, explain closed loop speed control of 3 phase induction motor. (05)
- OR**
- Q.5** Explain in detail static slip power recovery scheme for 3 phase induction motor. (10)
- Q.6** a) Explain load commutate inverter fed synchronous motor drive with circuit diagram. (05)
b) How to control the speed of synchronous motor by cyclo-converter? (05)
- OR**
- Q.6** Explain the current regulated VSI fed sinusoidal PMAC motor drive for servo application. Draw the closed loop diagram of it. (10)