

BACHELOR OF TECHNOLOGY (C.B.C.S.) (2021-COURSE)
B. Tech. Sem - I ELECTRICAL :SUMMER- 2022
SUBJECT : ELECTROMAGNETICS & ITS APPLICATIONS

Day : Wednesday
Date : 20-07-2022

S-24073-2022

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Assume suitable data **WHEREVER** necessary.

-
- Q.1** a) Explain with diagram Superposition Theorem. (05)
b) Explain with diagram Maximum Power Transfer Theorem. (05)

OR

- Q.1** a) Explain the concept of an electric network. (05)
b) Explain active and passive elements in D.C. circuit analysis. (05)

- Q.2** a) Explain Faraday's law of electromagnetic induction. State the concept of statically and dynamically induced EMF. (05)
b) Explain coefficient of Mutual Inductance. State sign and dot convention. (05)

OR

- Q.2** a) Explain the following terms : (05)
Flux, Flux Density, Field Strength.
b) Compare between electric and magnetic circuits. (05)

- Q.3** a) State the causes of low power factor. (05)
b) Elaborate the methods of power factor improvement. (05)

OR

- Q.3** a) Explain with reference to AC fundamentals following : (05)
Sinusoidal, square and triangular waveforms.
b) Describe with diagram concept of phasors. (05)

- Q.4** a) Explain the concept of balanced supply and balanced load in transformer connections. (05)
b) Explain line and voltage / current relations in star delta connections. (05)

OR

- Q.4** a) State the necessity and advantages of three phase systems. (05)
b) Explain the meaning of phase sequence. (05)

- Q.5** a) Explain losses in transformer. Describe the concept of ideal transformer. (05)
b) Explain the working of three phase transformer and its connections. (05)

OR

- Q.5** a) Explain with diagram the construction of single phase transformer. (05)
b) Explain with diagram principle of operation of single phase transformer. (05)

- Q.6** a) Write short note on parallel operation of single phase transformer. (05)
b) Write short note on open circuit or no-load test of transformer. (05)

OR

- Q.6** a) Explain the working of single phase transformer on no-load. (05)
b) Write short note on efficiency of single transformer. (05)
